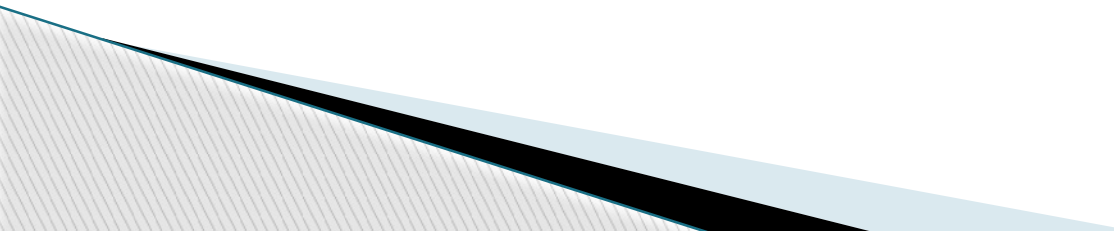




Stafford and Districts  
Amateur Radio Society



# Resistance is ~~Futile~~ Crucial


- ▶ What are they?
  - ▶ What do they do?
  - ▶ How are they used?
  - ▶ Types, Values, Tolerance
- 





# What are they?






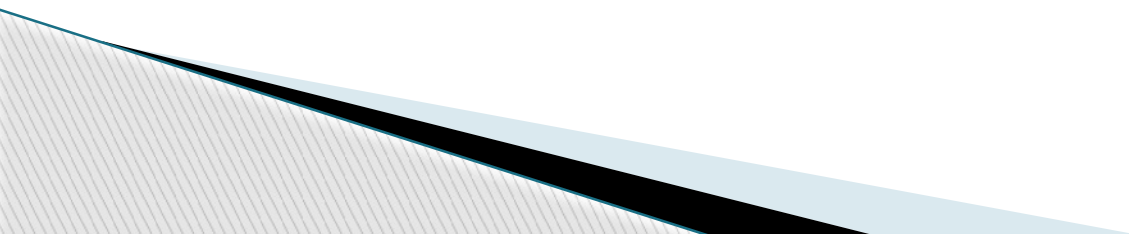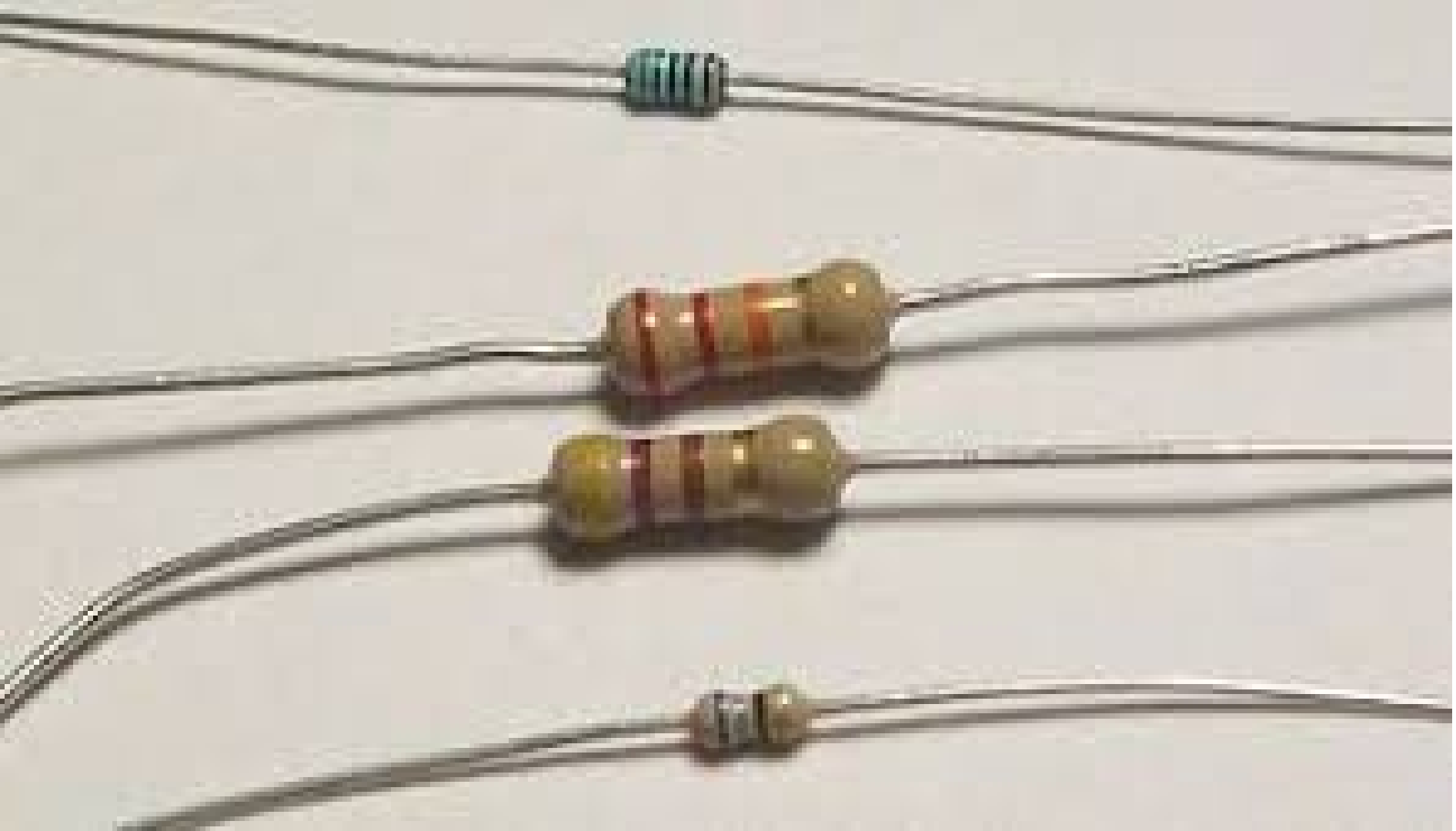

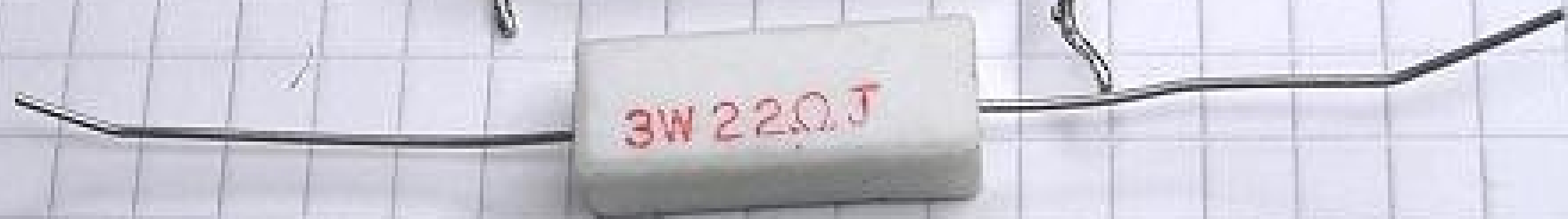


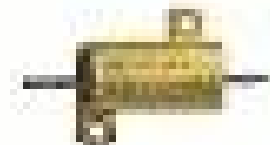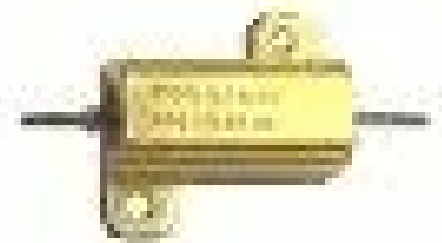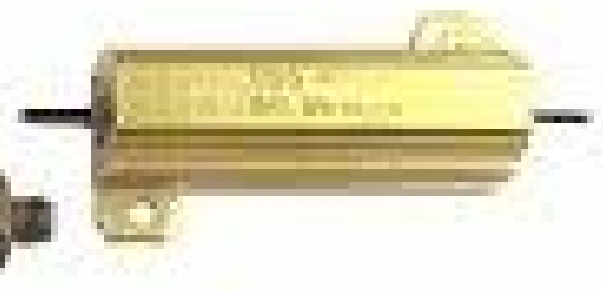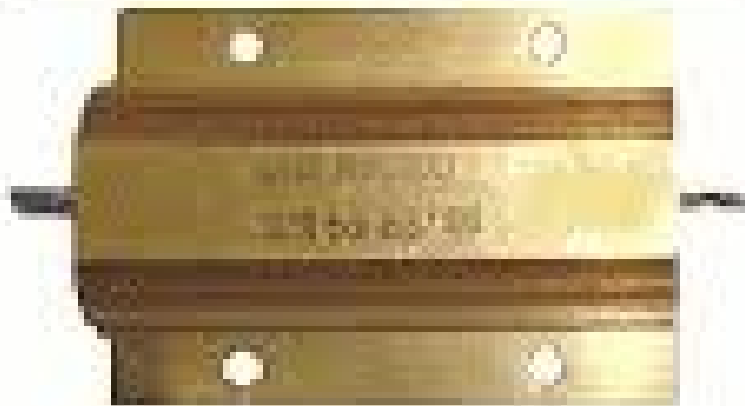

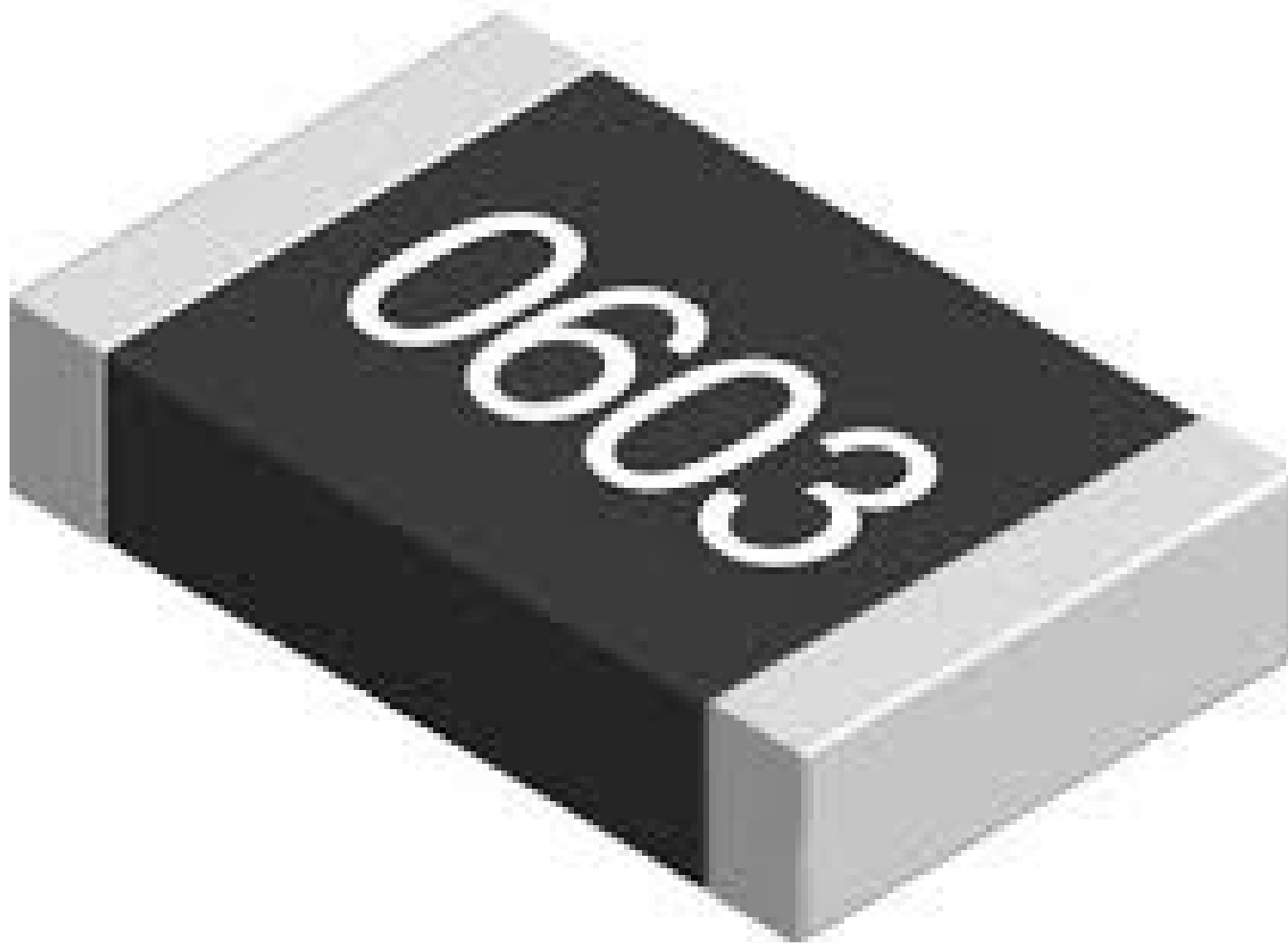

Package type	Size in inches	Size in mm	Power rating
0201	0.024" × 0.012"	0.6 mm × 0.3 mm	1/20W
0402	0.04" × 0.02"	1.0 mm × 0.5 mm	1/32W 1/16W
0603	0.063" × 0.031"	1.6 mm × 0.8 mm	1/16W
0805	0.08" × 0.05"	2.0 mm × 1.25 mm	1/10W
1206	0.126" × 0.063"	3.2 mm × 1.6 mm	1/8W
1210	0.12" × 0.10"	3.2 mm × 2.6 mm	1/4W
2020	0.20" × 0.20"	5.08 mm × 5.08 mm	1/2W
2512	0.25" × 0.12"	6.35 mm × 3.0 mm	1W

# What are they made of?

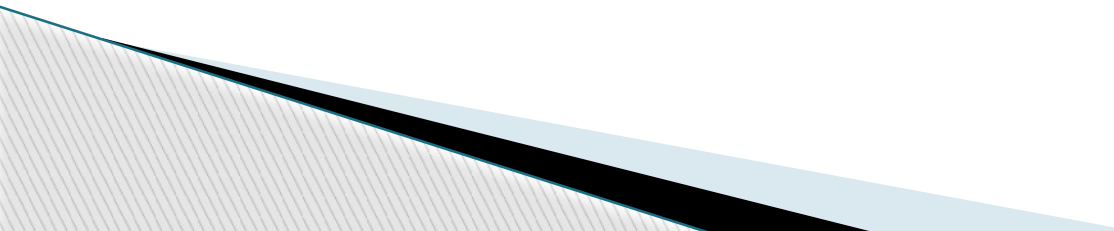
- ▶ Carbon
  - ▶ Metal film
  - ▶ Metal oxide (MOX)
  - ▶ Resistance Wire
- 

# What do they do?


- ▶ Pass a current, depending on the voltage applied.
- ▶ Define voltage at a point in a circuit.
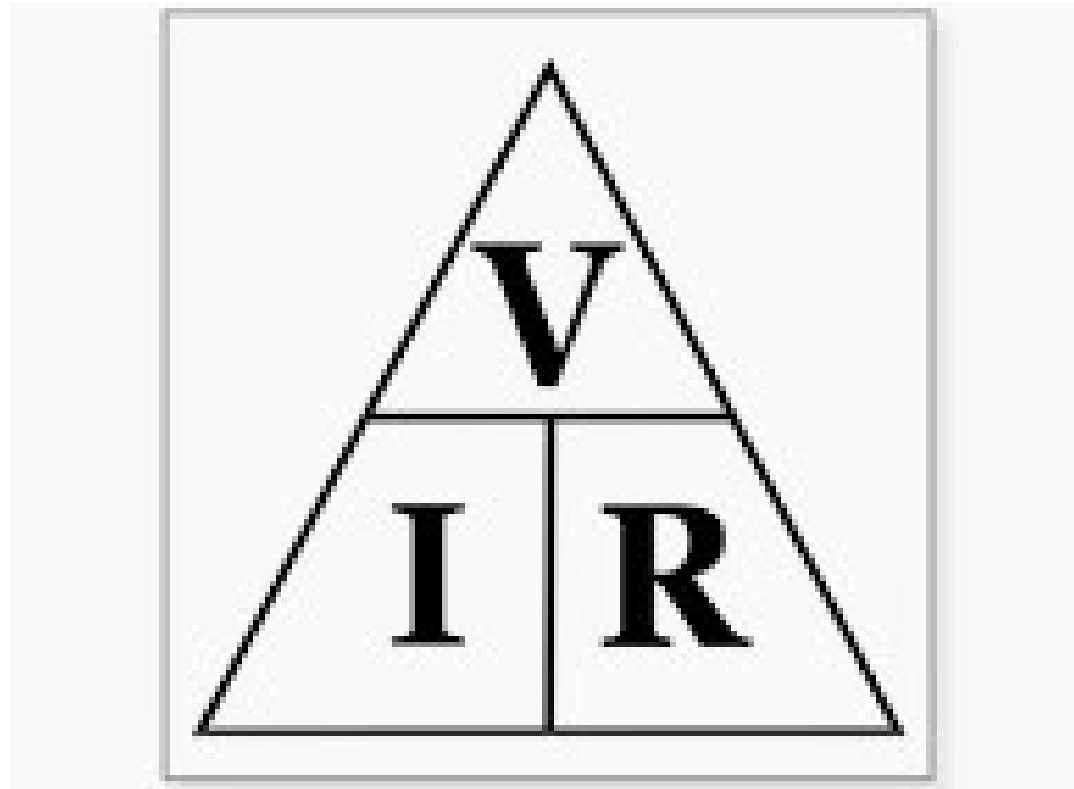
# Ohm's Law

▶  $V = I \times R$      $I = V / R$      $R = V / I$







# What's with the colours?

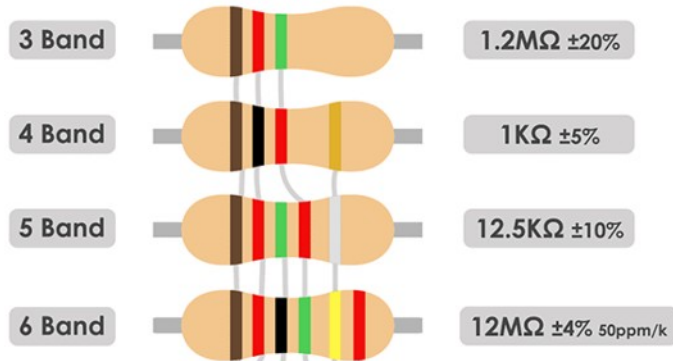

	1 <sup>st</sup> Digit	2 <sup>nd</sup> Digit	3 <sup>rd</sup> Digit	Multiplier	Tolerance	Temp. Coeff.
Black	0	0	0	$\times 10^0$		250 (U)
Brown	1	1	1	$\times 10^1$	±1%	100 (S)
Red	2	2	2	$\times 10^2$	±2%	50 (R)
Orange	3	3	3	$\times 10^3$	±3%	15 (P)
Yellow	4	4	4	$\times 10^4$	±4%	25 (Q)
Green	5	5	5	$\times 10^5$	±0.5%	20 (Z)
Blue	6	6	6	$\times 10^6$	±0.25%	10 (Z)
Violet	7	7	7	$\times 10^7$	±0.1%	5 (M)
Grey	8	8	8	$\times 10^8$	±0.05%	1 (K)
White	9	9	9	$\times 10^9$		
Gold	-	-	-	$\times 10^{-1}$	±5%	
Silver	-	-	-	$\times 10^{-2}$	±10%	


Codrey Electronics

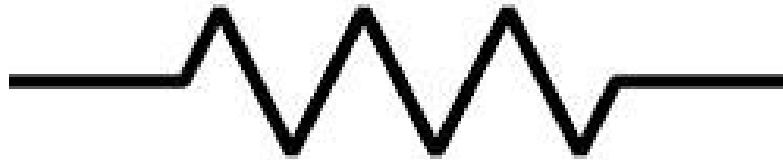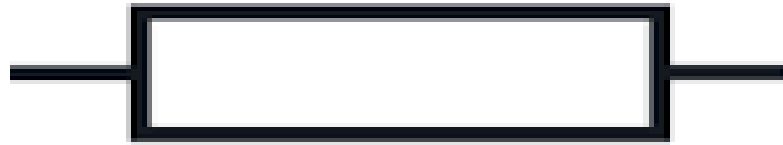 

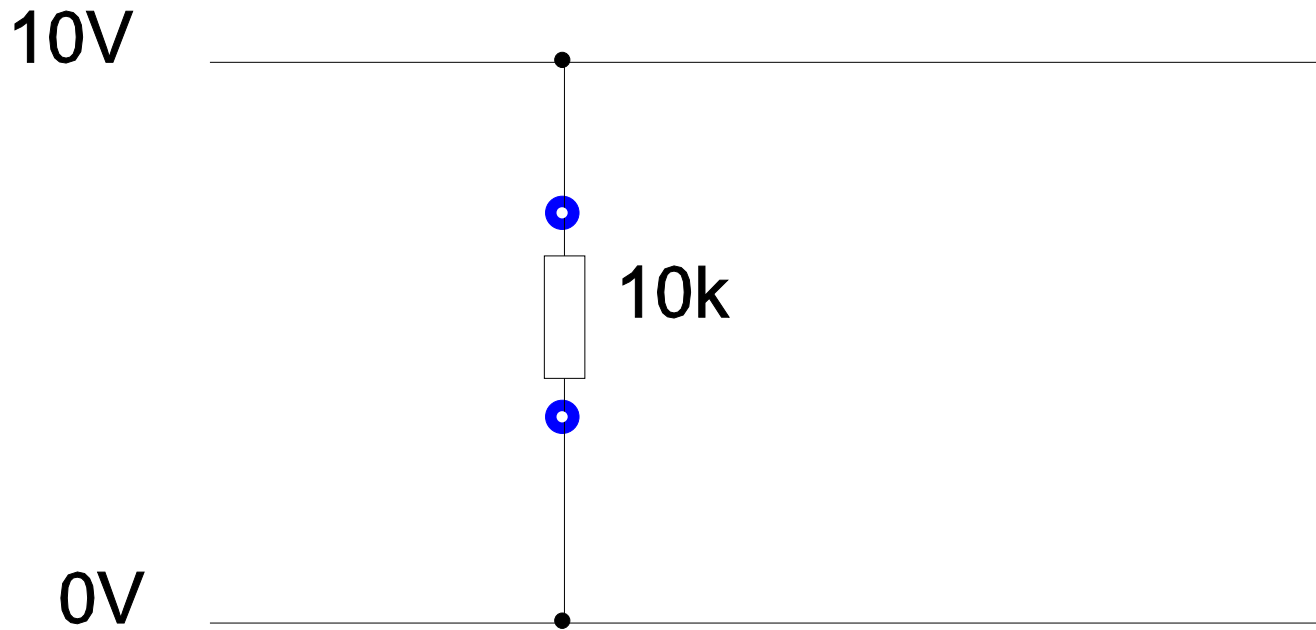


$$10\text{V}/10,000\text{R} = 0.001\text{A} (1\text{mA})$$

# Potentiometer

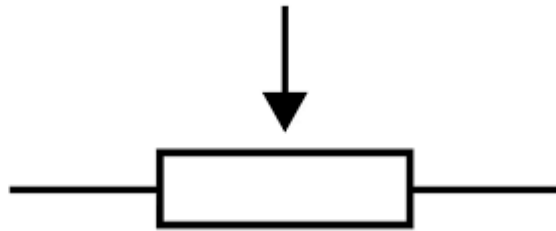


European standard (IEC)

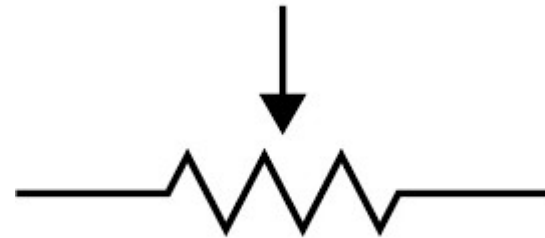

American standard (ANSI)

# Potential (Voltage) divider

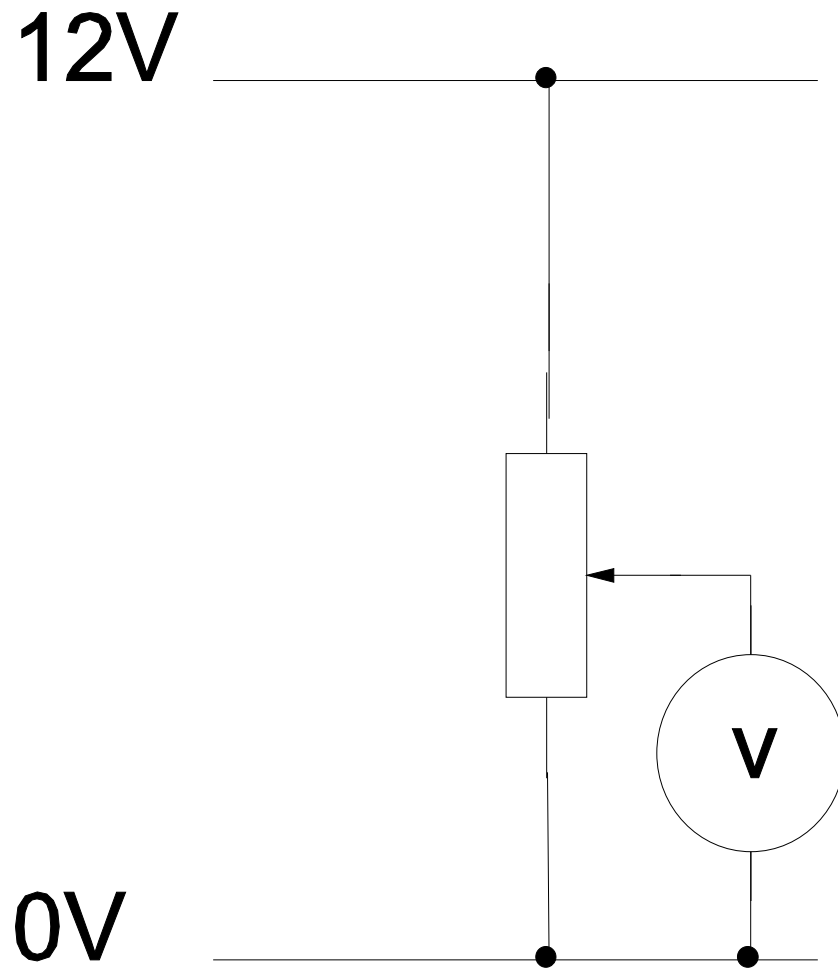

10V



5k



5k



$5k+5k=10k$


0V



$10V/10,000R = 0.001A (1mA)$


# Series connection

R total

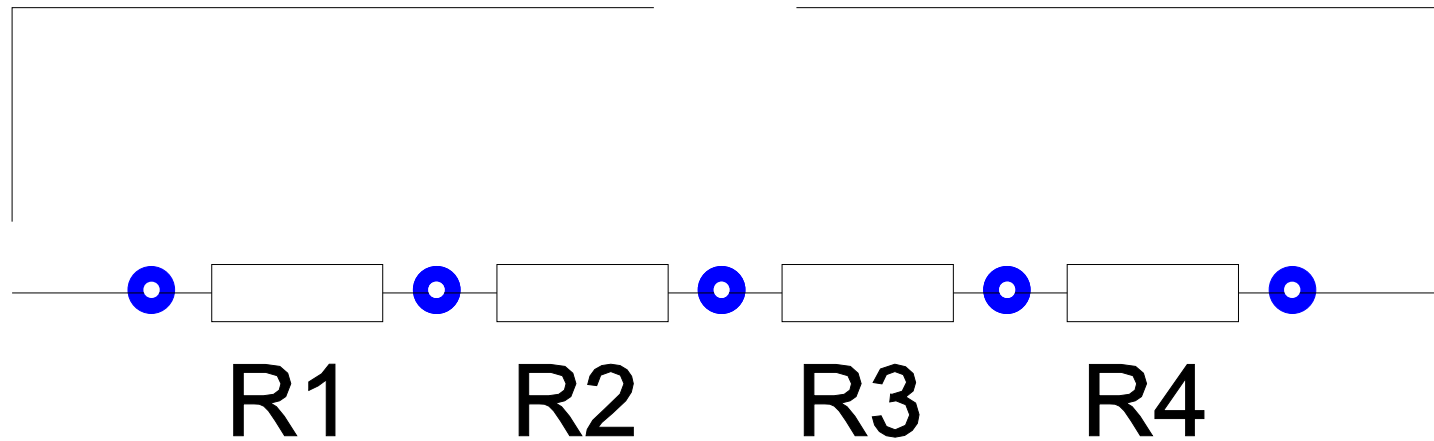


$$R \text{ total} = R1 + R2 + R3 + R4$$

# Parallel connection

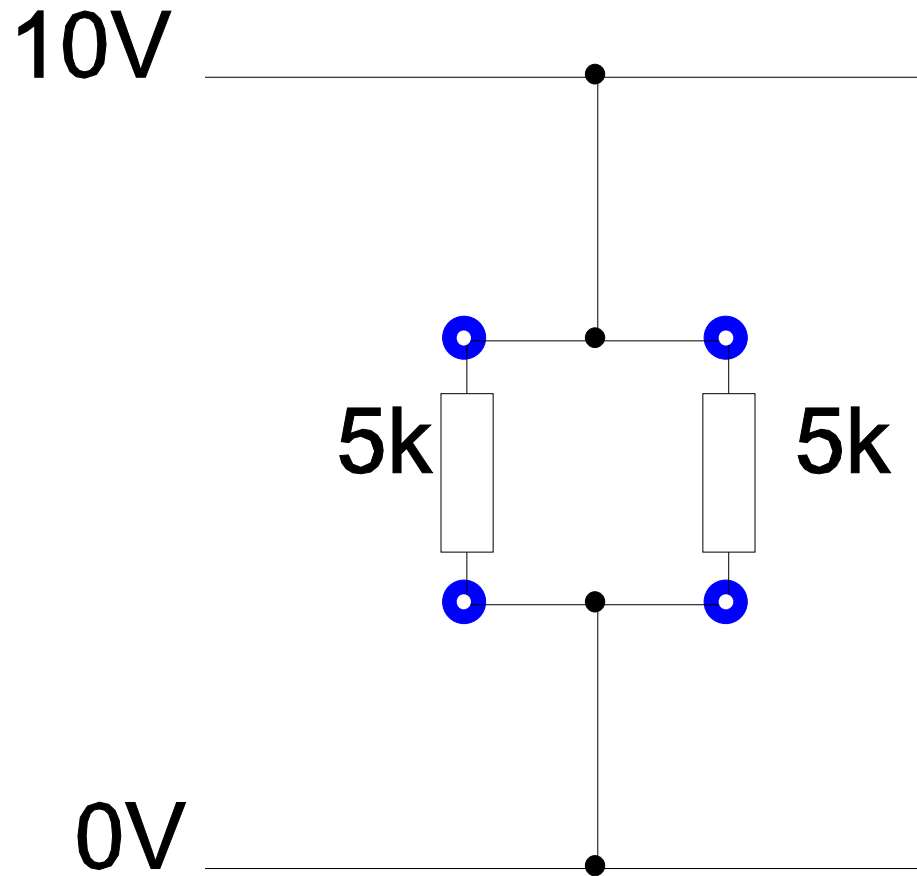

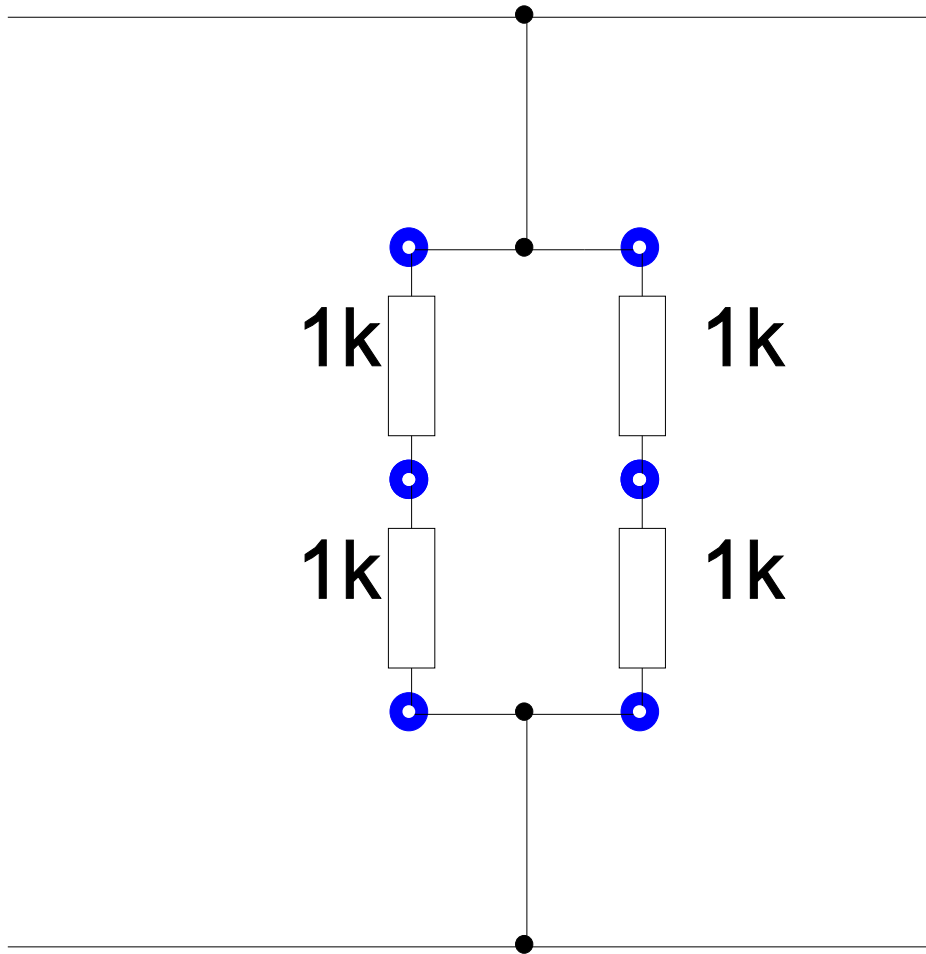
# Parallel connection

- ▶  $1/R_{\text{total}} = 1/5k + 1/5k$
- ▶  $R_{\text{total}} = R_1 \times R_2 / (R_1 + R_2)$



?

# Attenuator

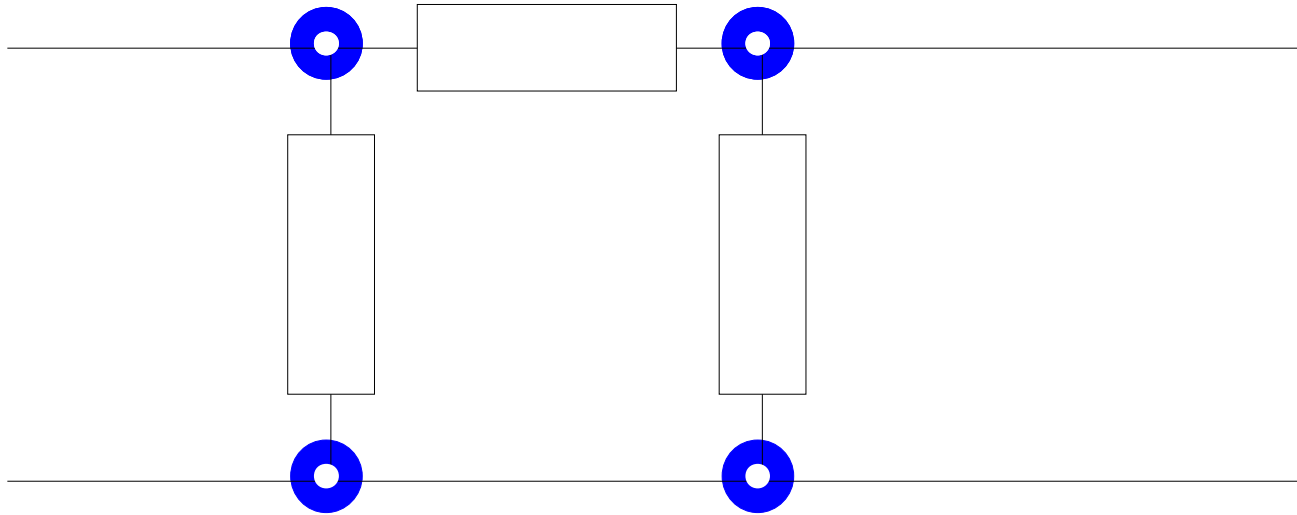

# Filter

