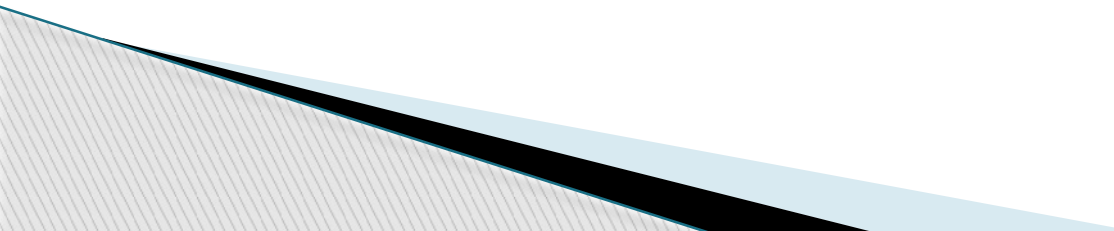


Diodes



Aim

- ▶ Basic theory
 - ▶ Types
 - ▶ Tricks / Applications
- 

Silicon

LED

Germanium

Gunn

Avalanche

Step Recovery

ZENER

PIN

SCHOTTKY

Back

SIGNAL


RECTIFIER

VARACTOR
(VARICAP)

Tunnel

Laser


Photo

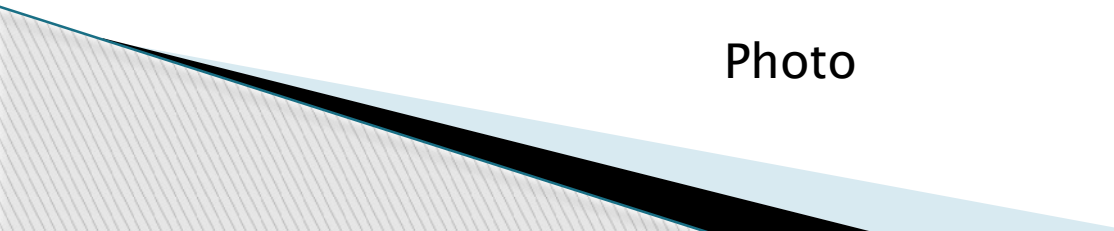


BASIC THEORY




The P-N Junction

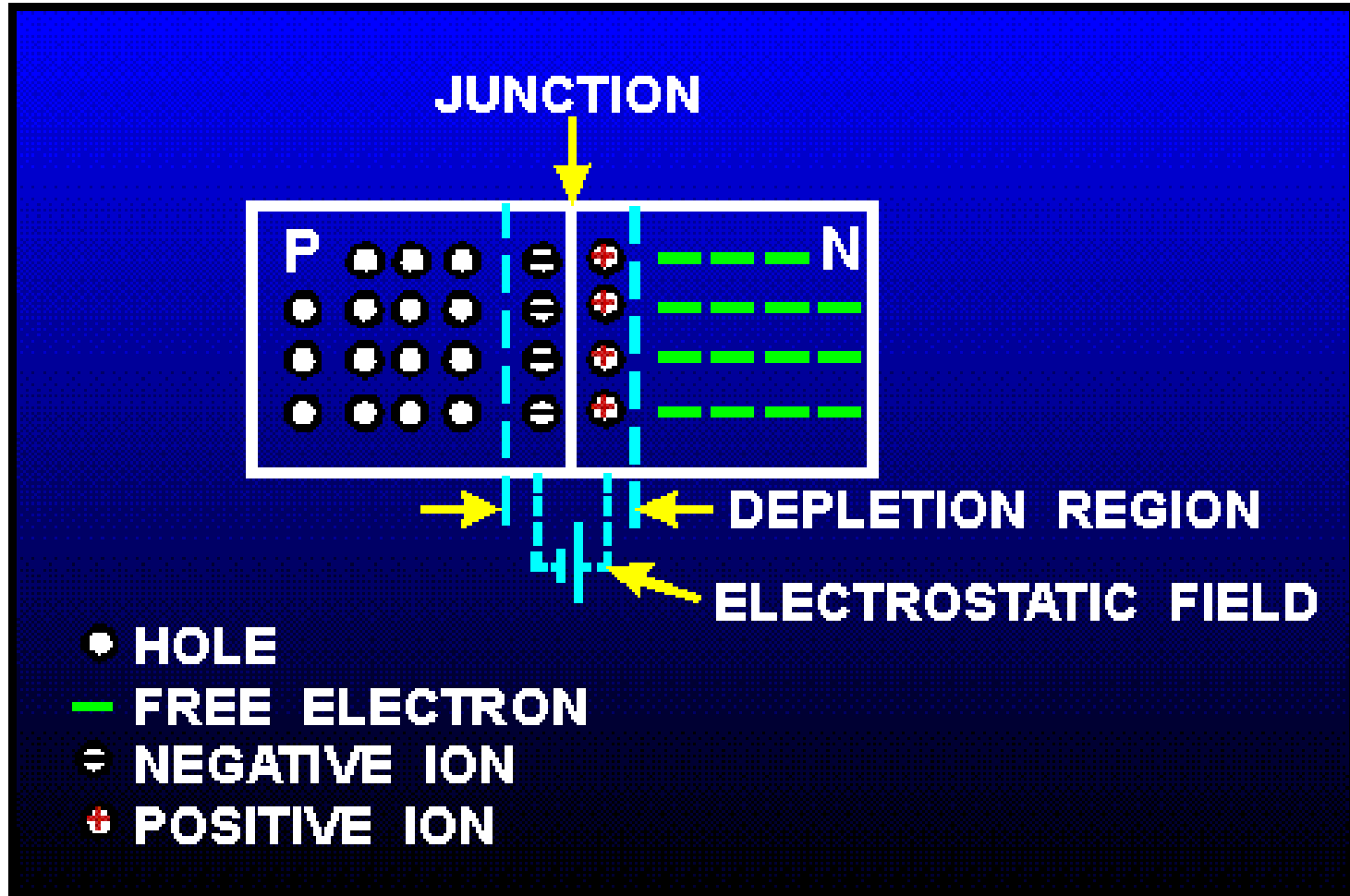


The P-N Junction

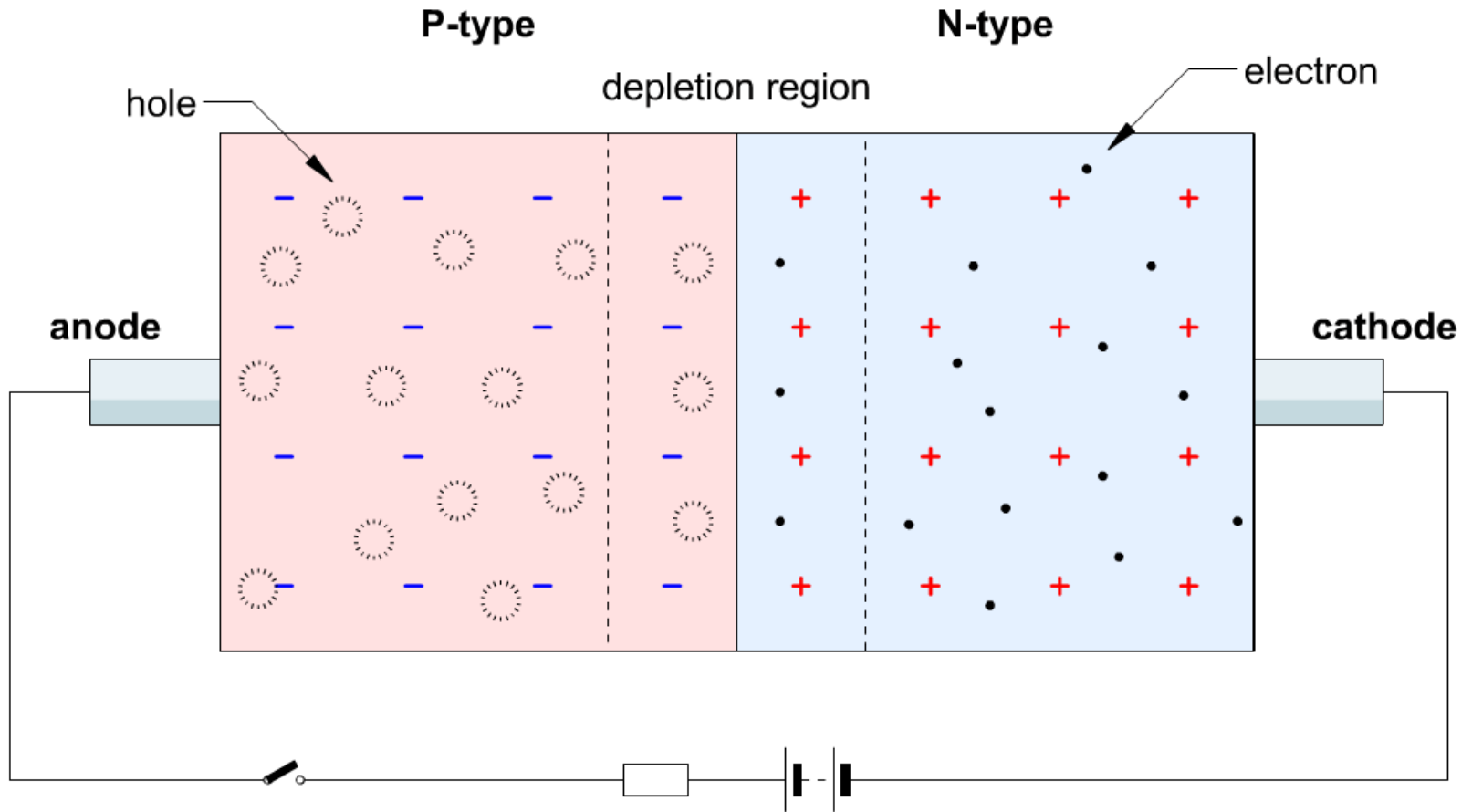


The P-N Junction

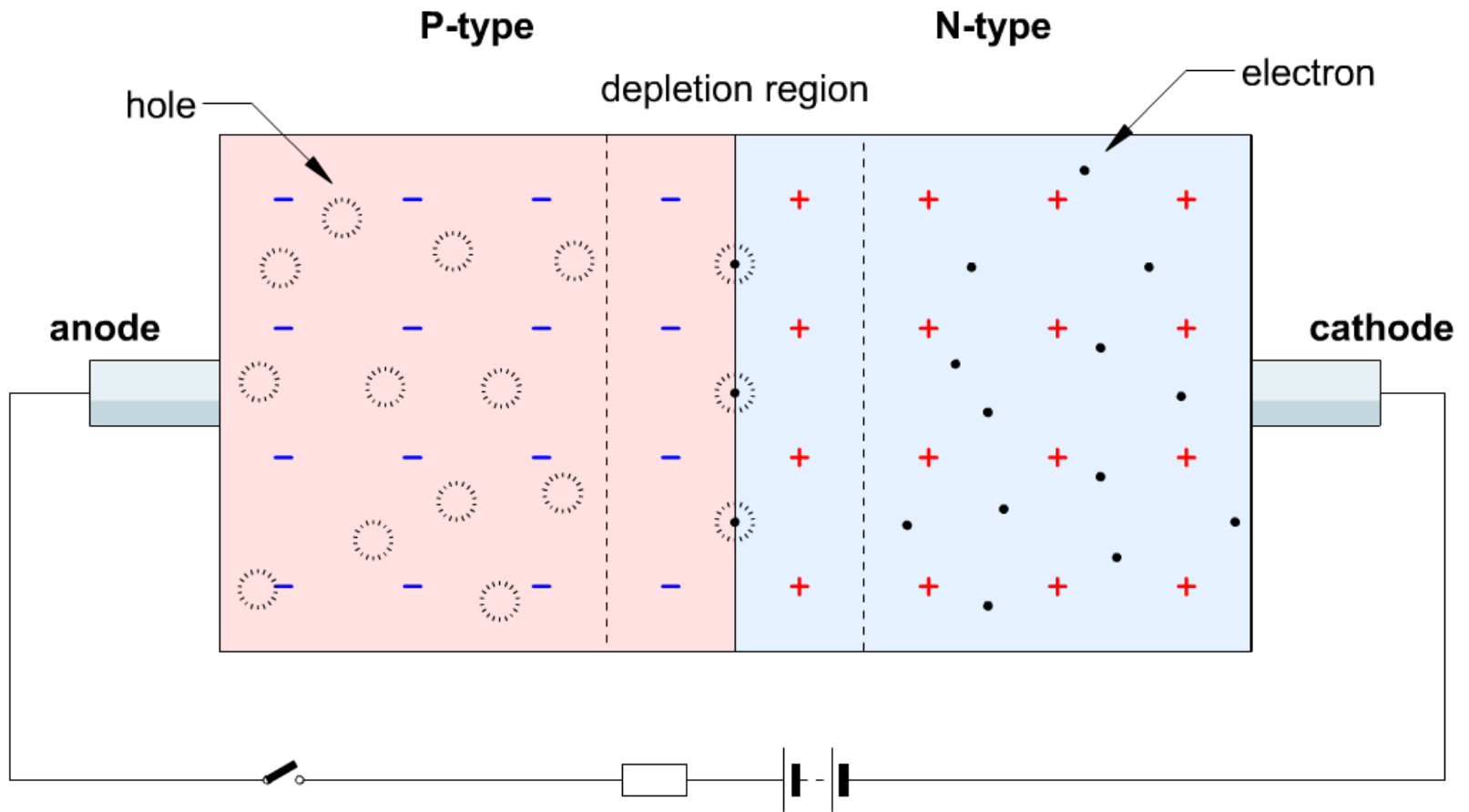


The P-N Junction

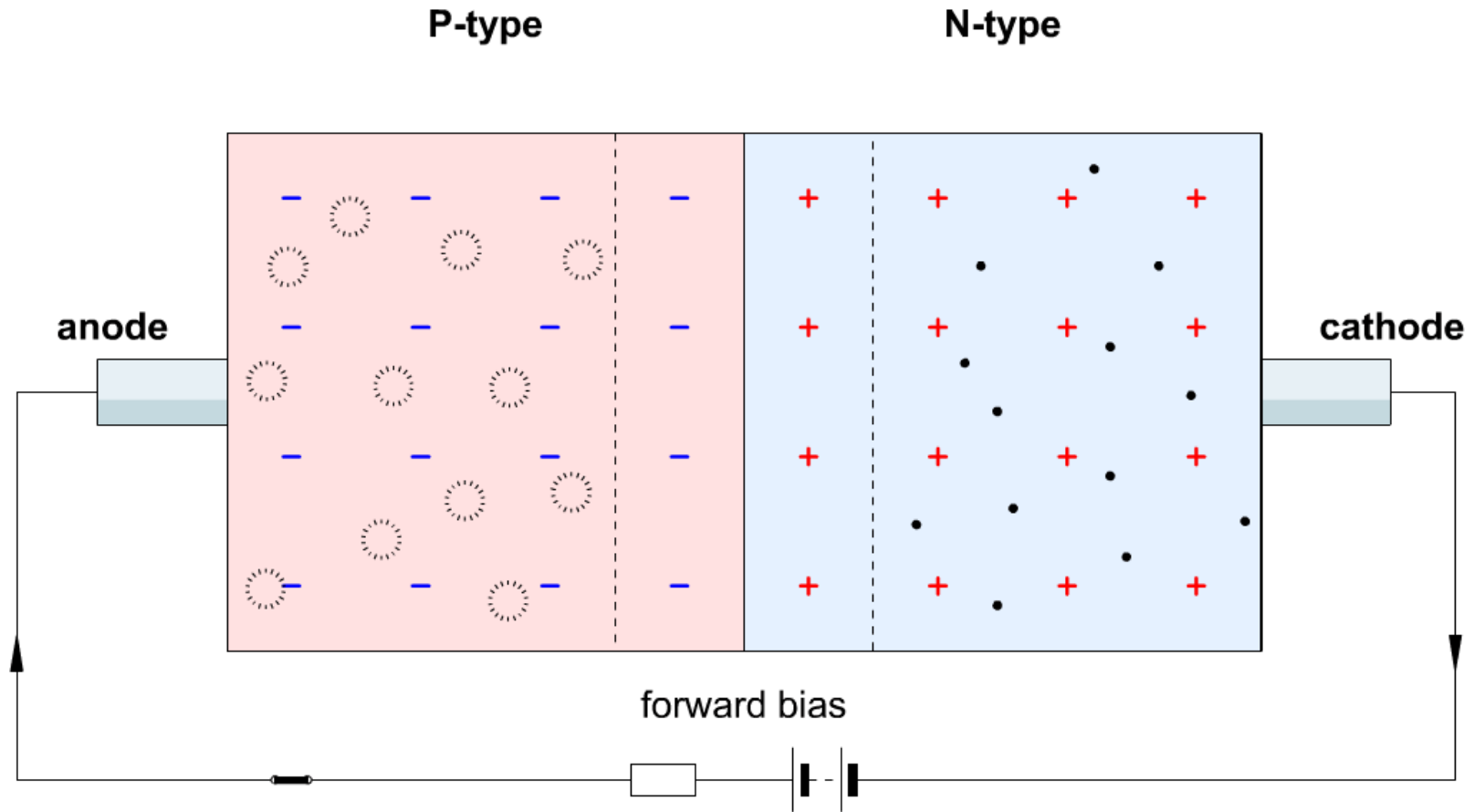


The P-N Junction

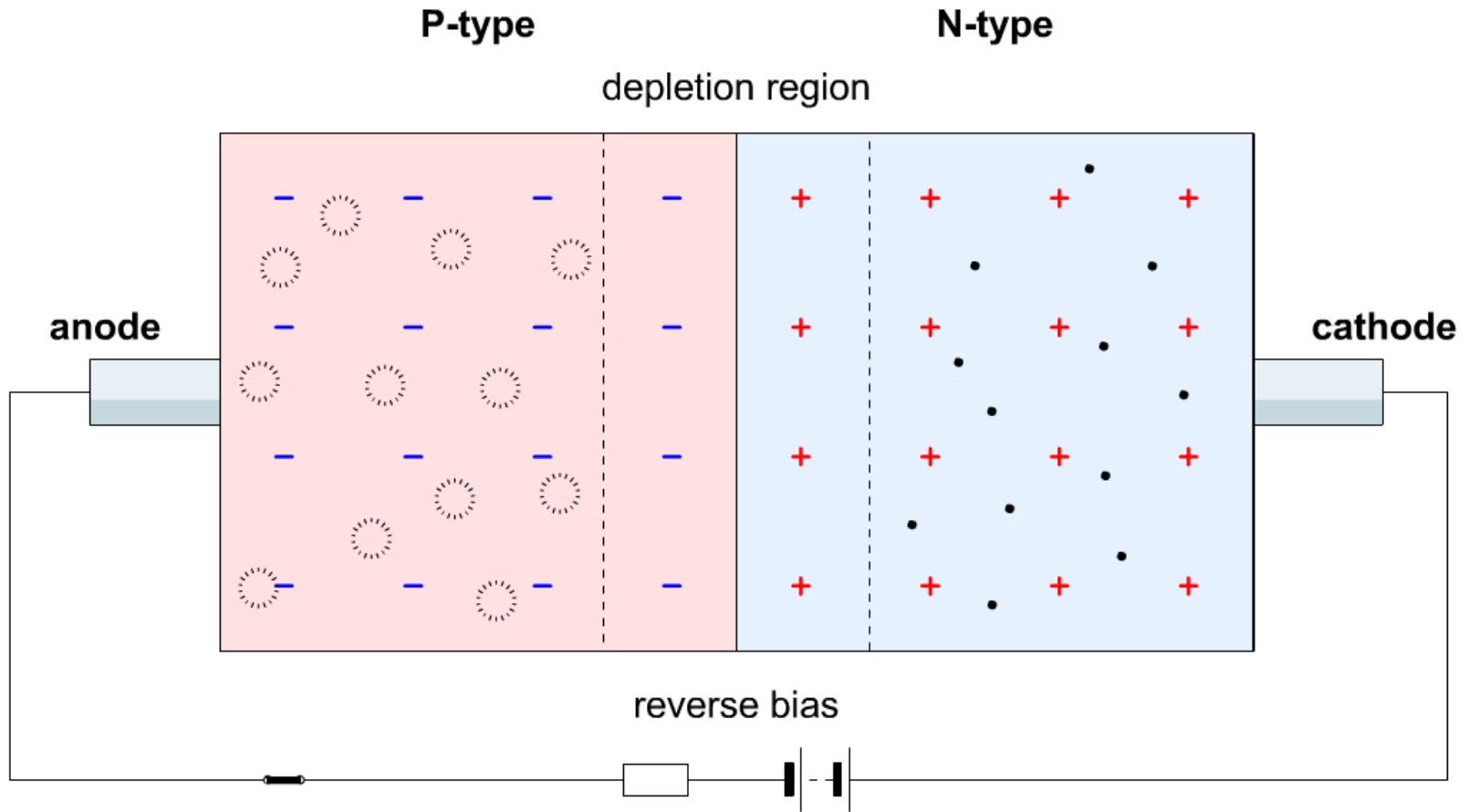

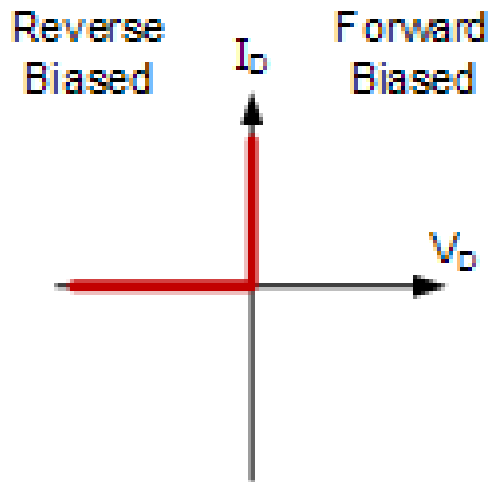


Ideal Diode

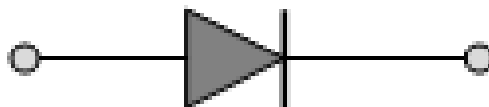



Forward Biased




Reverse Biased

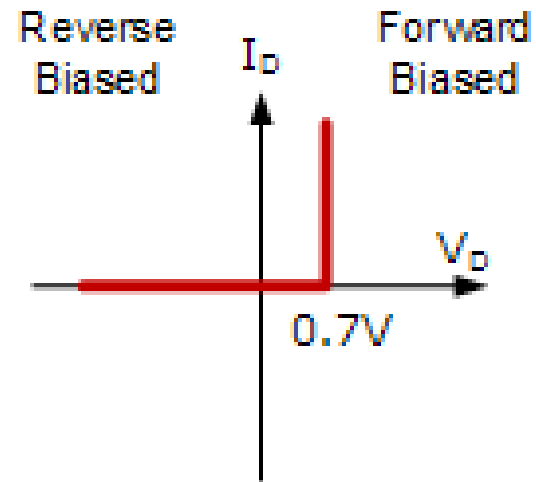

Real Diode

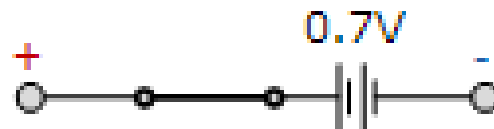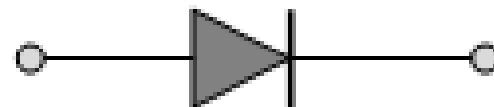

Forward Biased

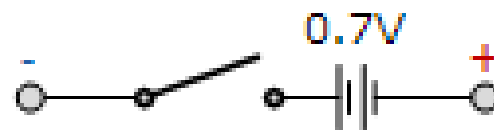


Reverse Biased

Conventional Current Flow




Anode


Cathode

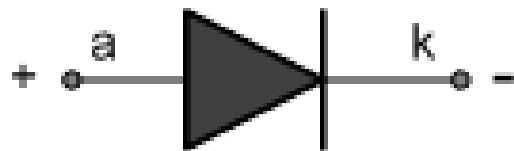

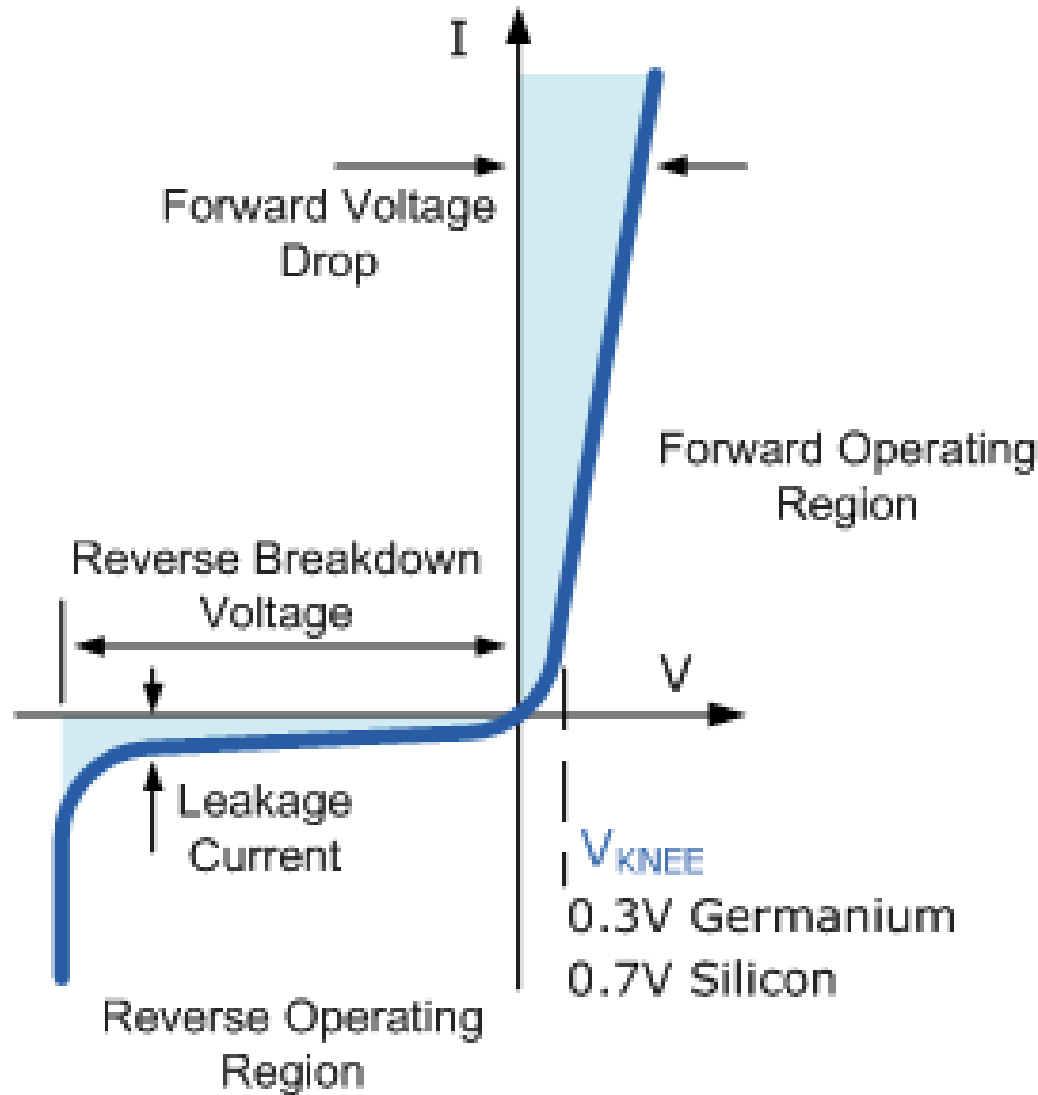Silicon Diode and its V-I Characteristics



DIODE TYPES

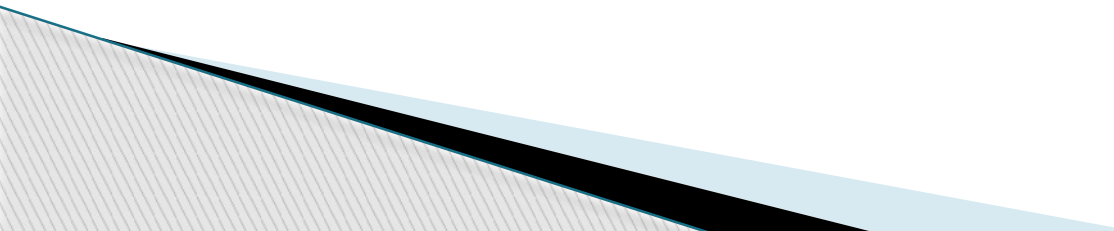- ▶ Silicon (NOT Silicone)
 - ▶ Germanium
 - ▶ Junction
 - ▶ Point contact
 - ▶ Varicap (varactor)
 - ▶ Zener
 - ▶ PIN
 - ▶ Schottky
- 


Common Types: Rectifiers



1N4001



Bridge Diode

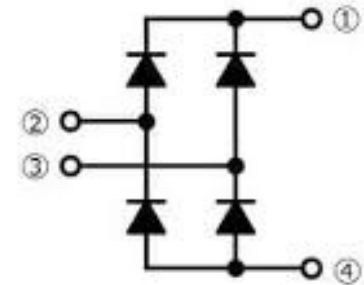

Common Types

Signal




1N914




1N4148

Junction Diode

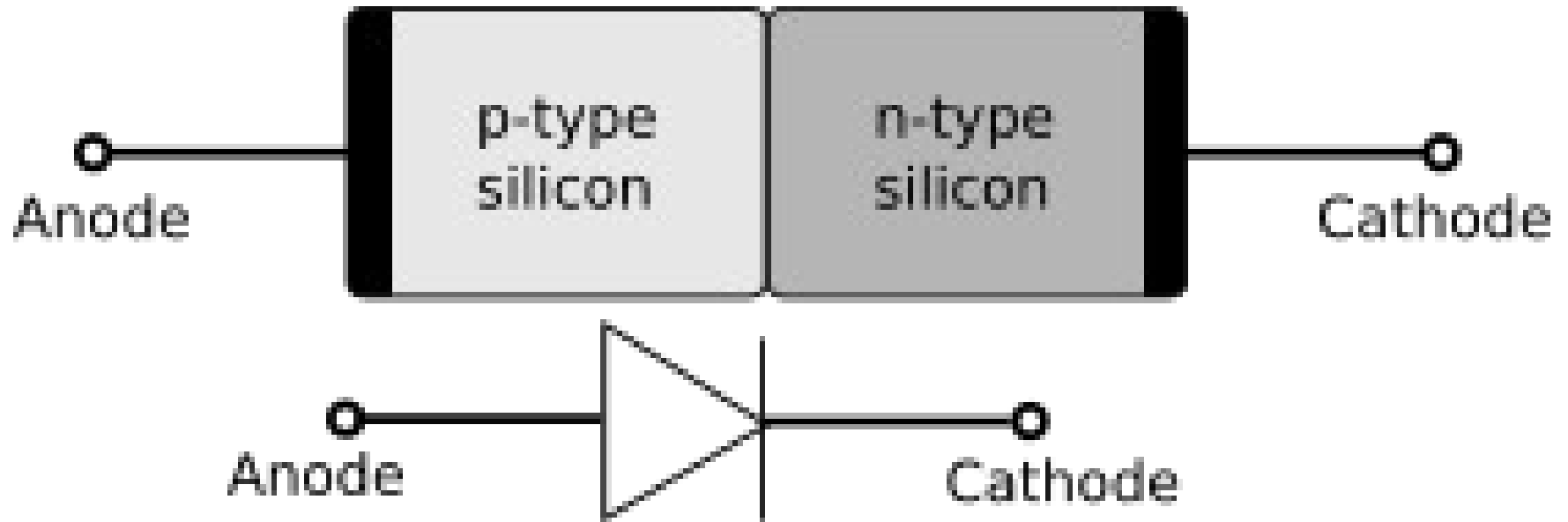


Point Contact Diode



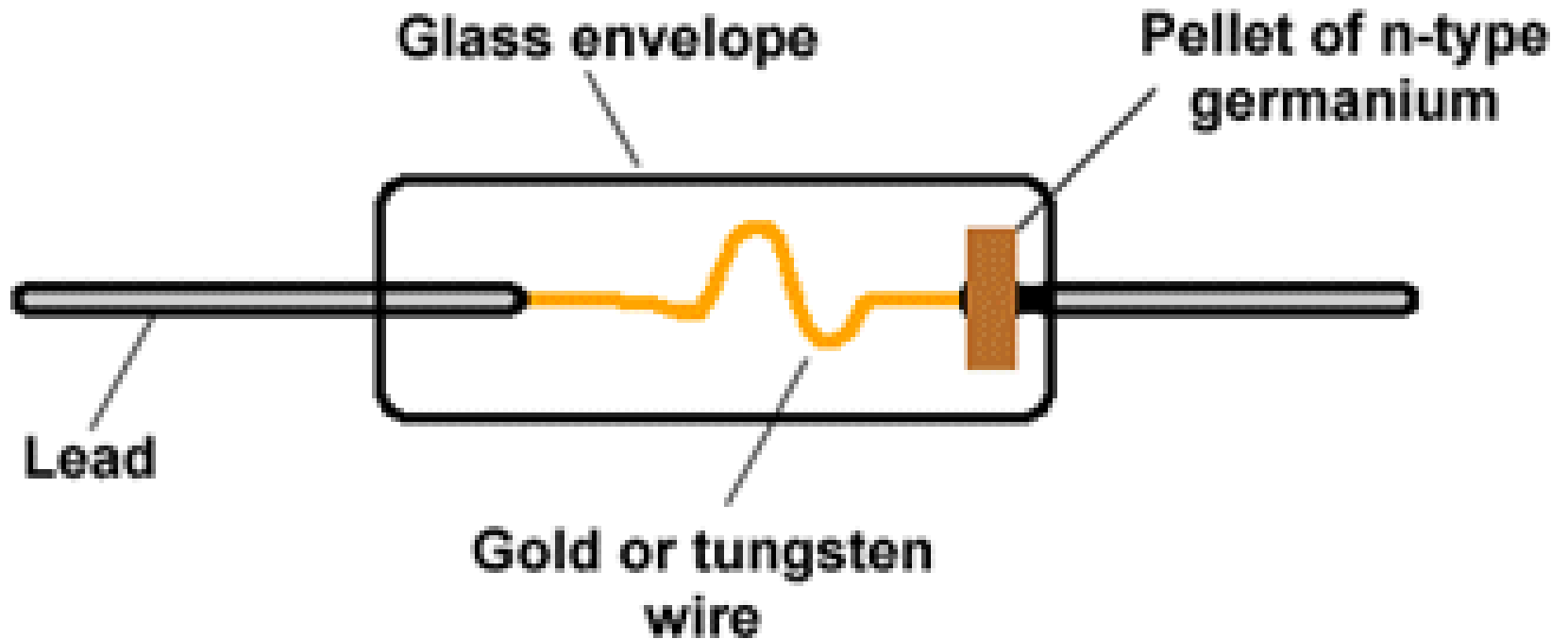




Point Contact Diode






What do they do?

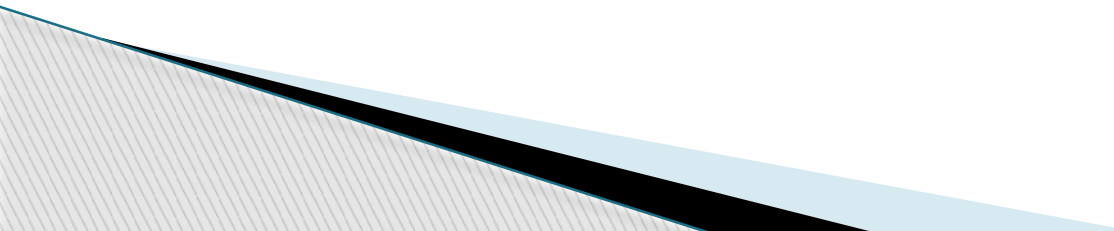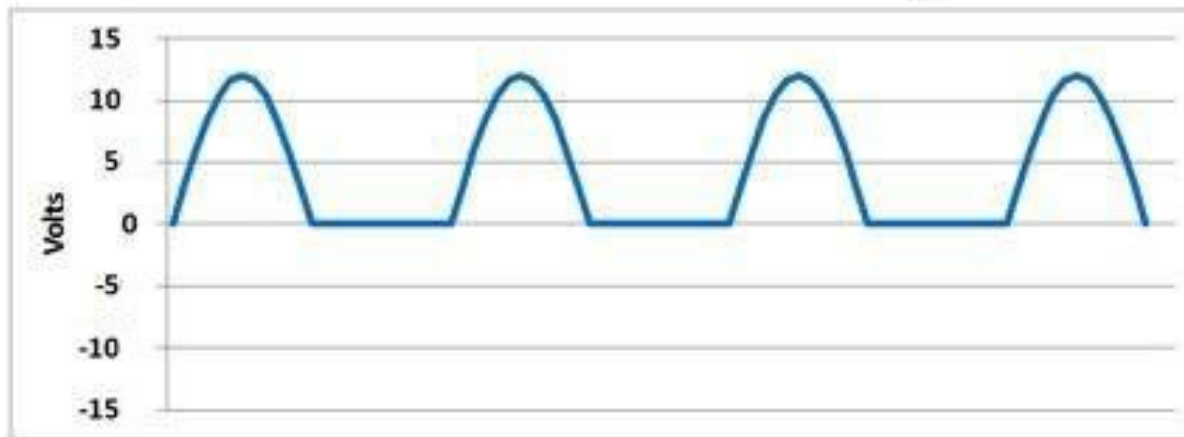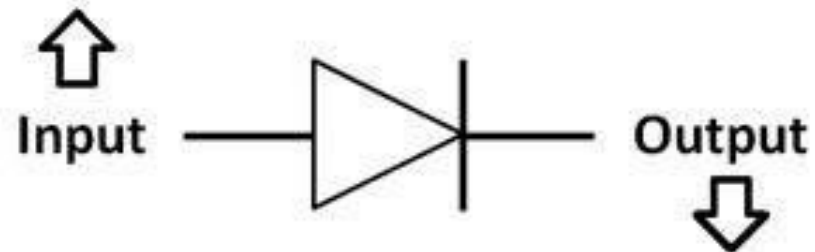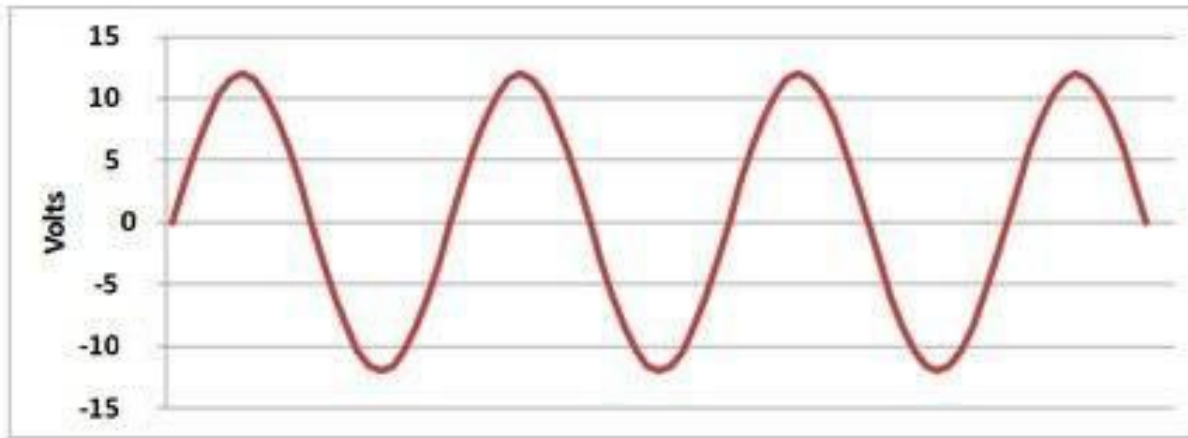
- ▶ Rectification
 - ▶ Switching
 - ▶ Signal steering
 - ▶ Voltage regulation
 - ▶ Protection
 - ▶ Tuning
- 



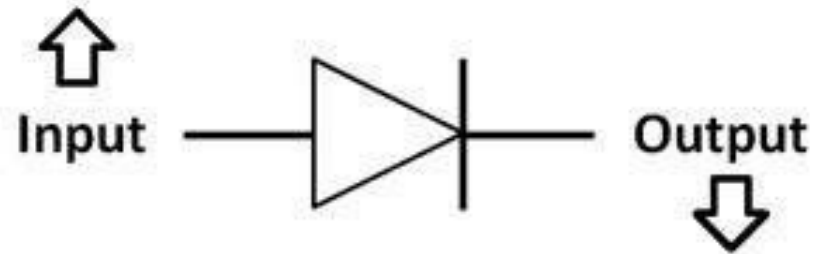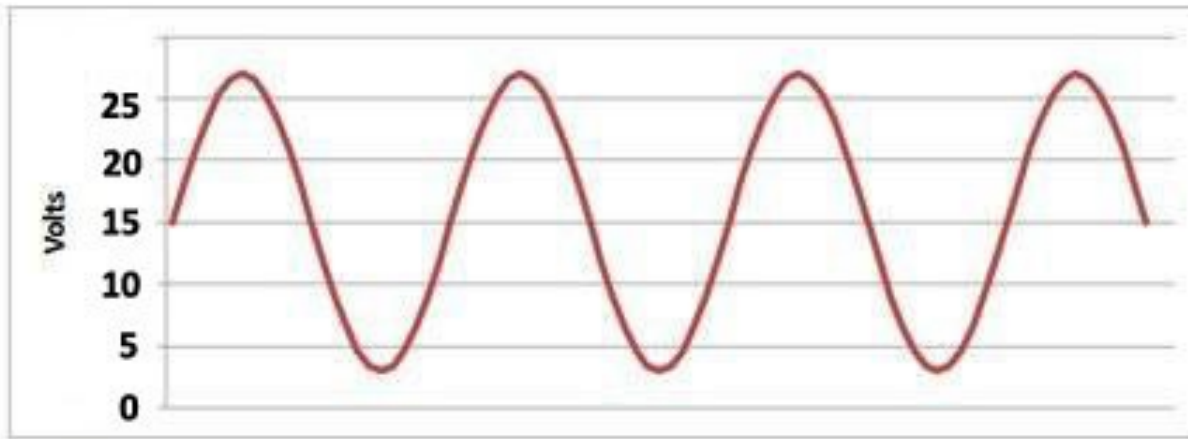


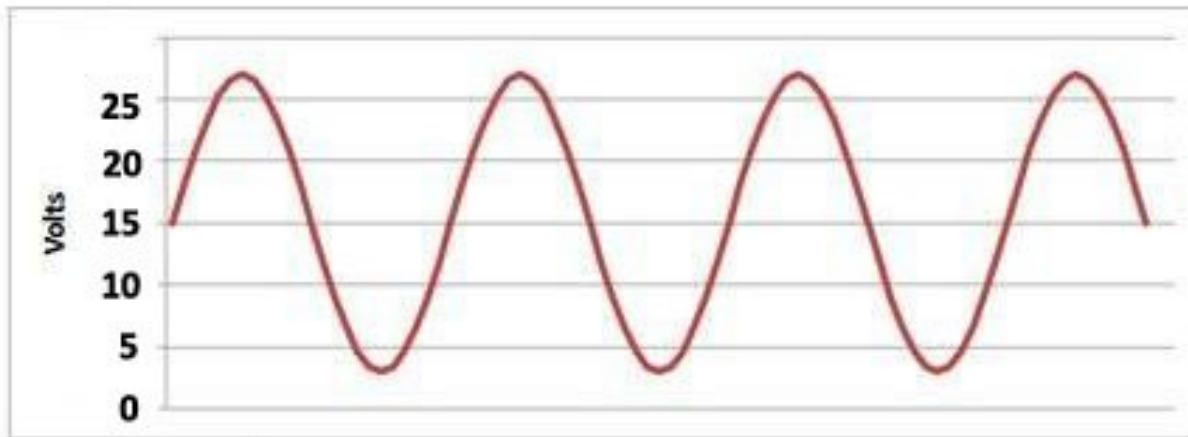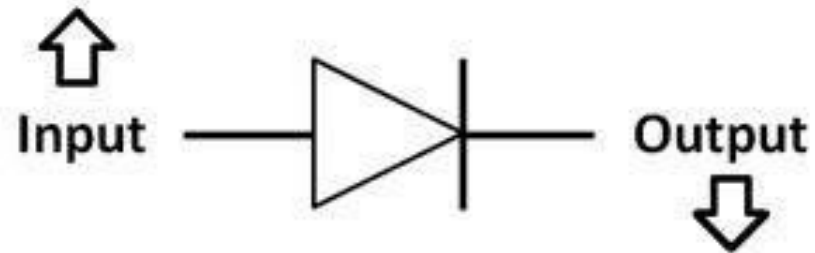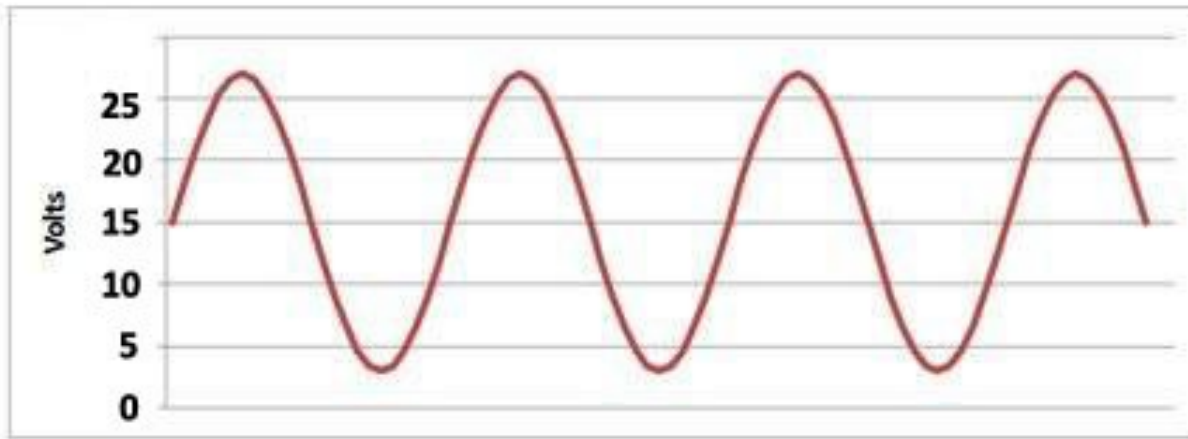

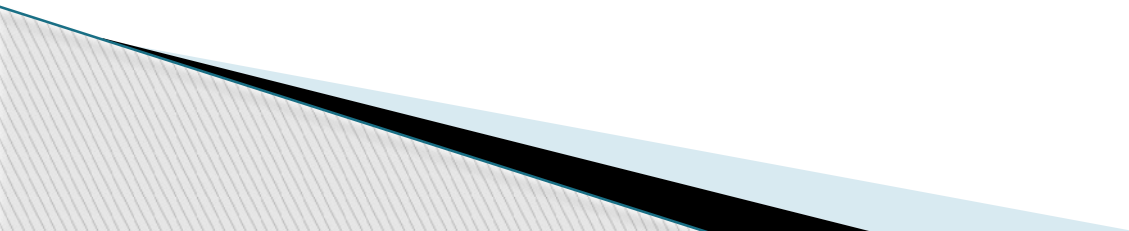
**A forward biased diode will
conduct in both directions**




Varicap Diode (Varactor)

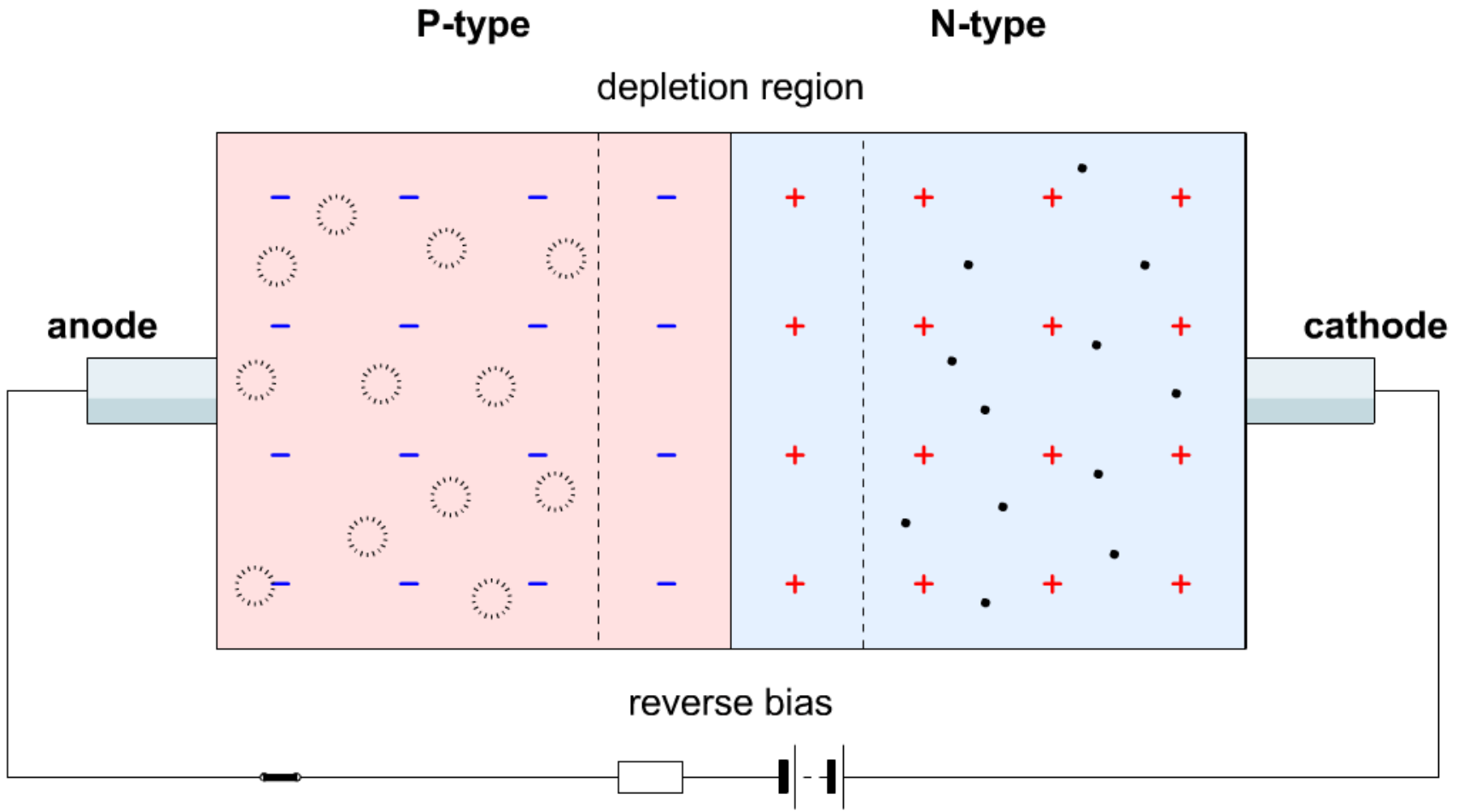


Varicap Diode

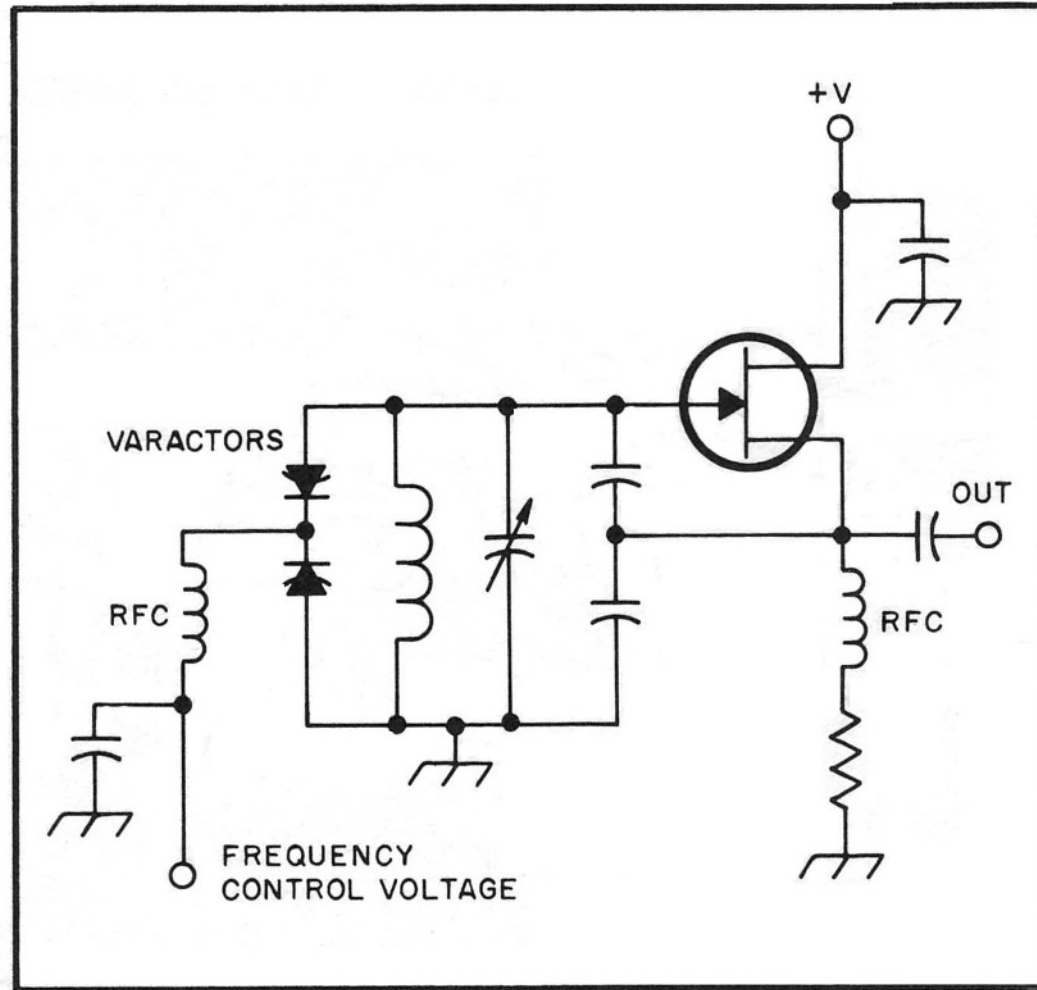


Varicap Diode (Varactor)

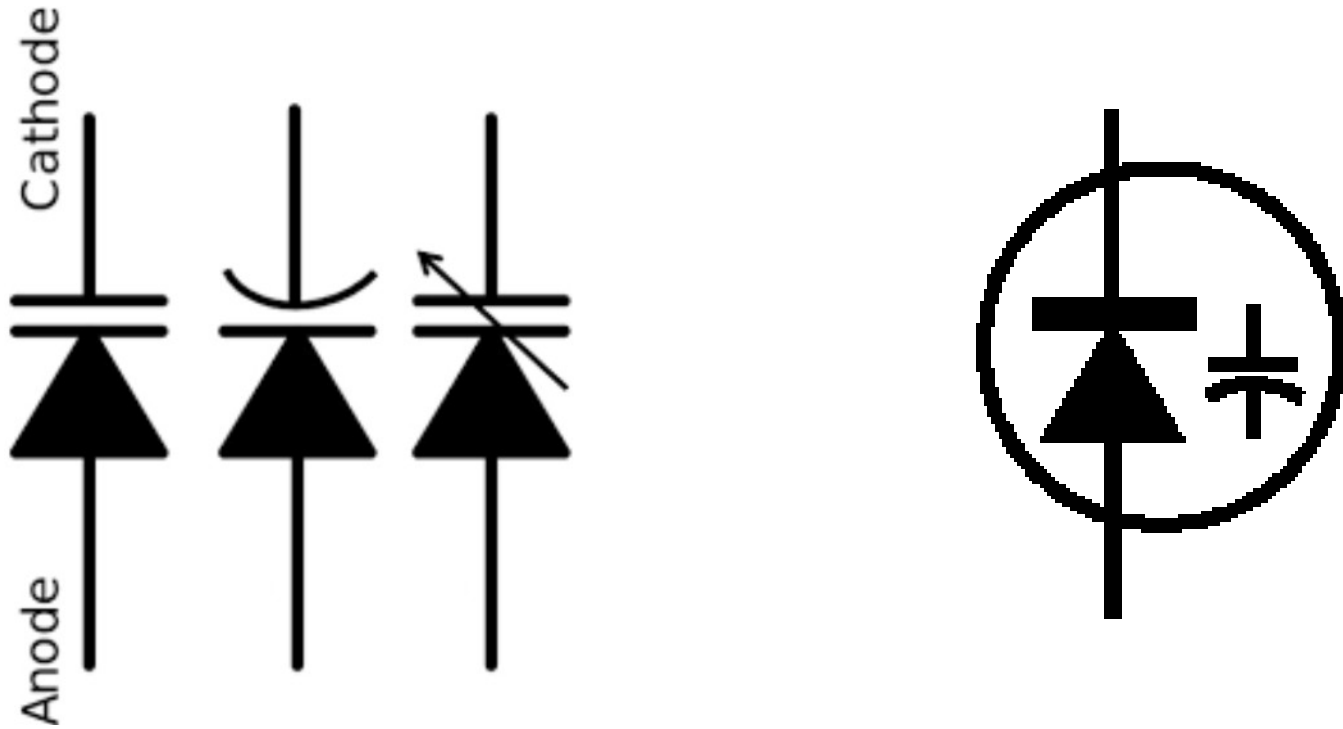

Zener Diode

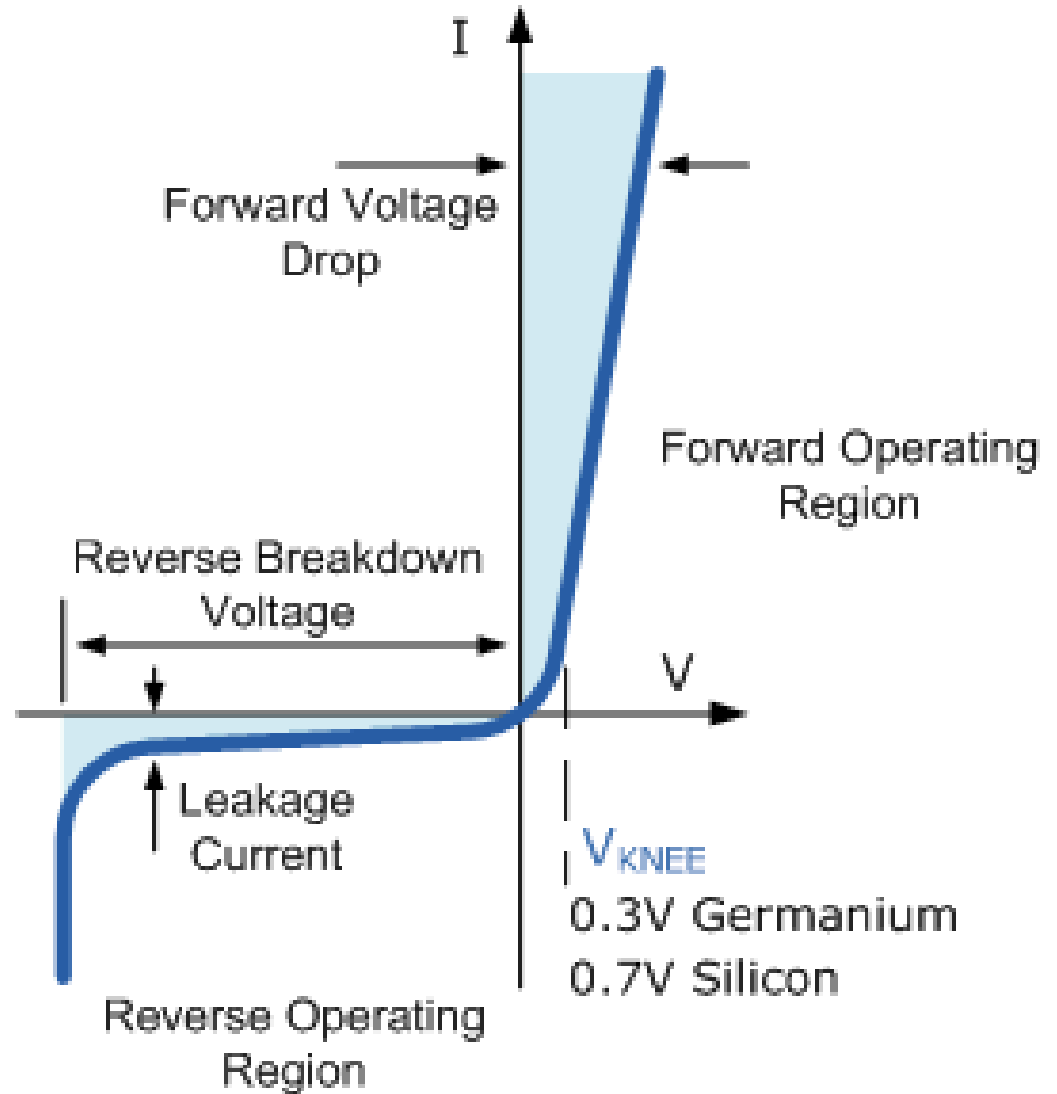


Avalanche Diode

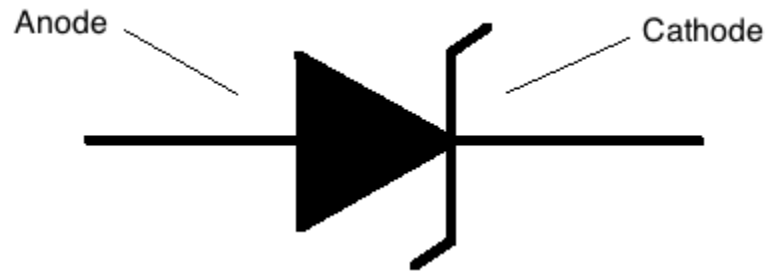

PIN Diode

- ▶ P type / Intrinsic / N type

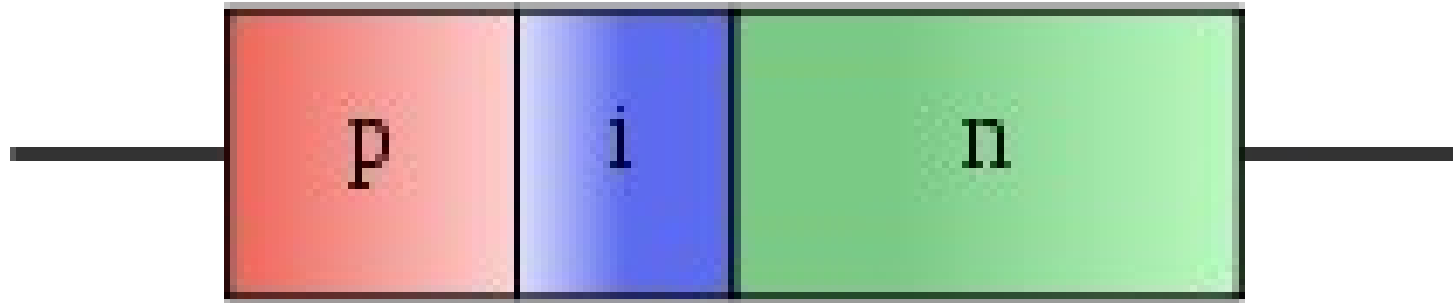


PIN Diode Applications

- ▶ RF Switching
- ▶ Attenuators

Schottky Diode

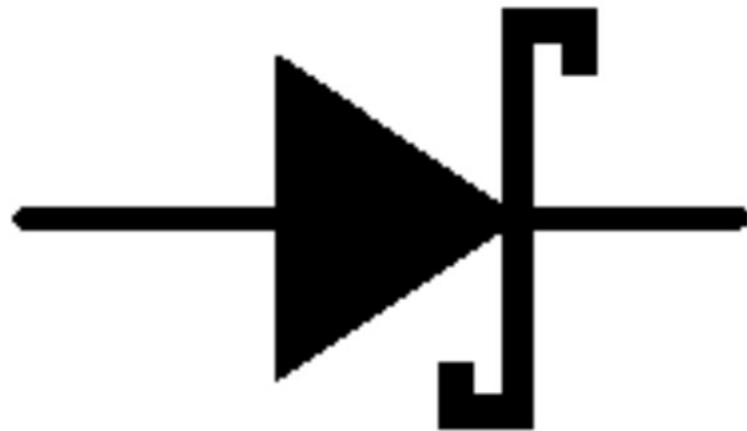- ▶ Metal to Semiconductor Junction
- ▶ N type silicon
- ▶ Hot Carrier Diode
- ▶ Used at RF , Fast Switching
- ▶ Low V_f – Reverse polarity protection




Applications

- ▶ Switching
 - ▶ Diode Matrix
 - ▶ Protection
-
- ▶ Bias tee


Switching

- ▶ Cheap
- ▶ DC controlled

Switching

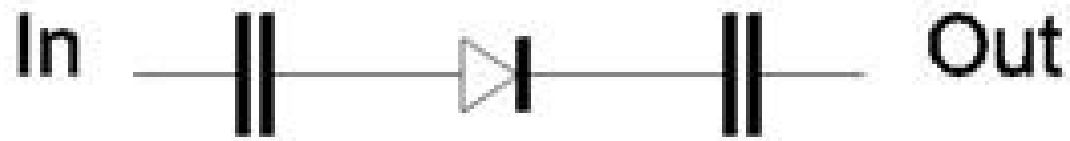



Switching

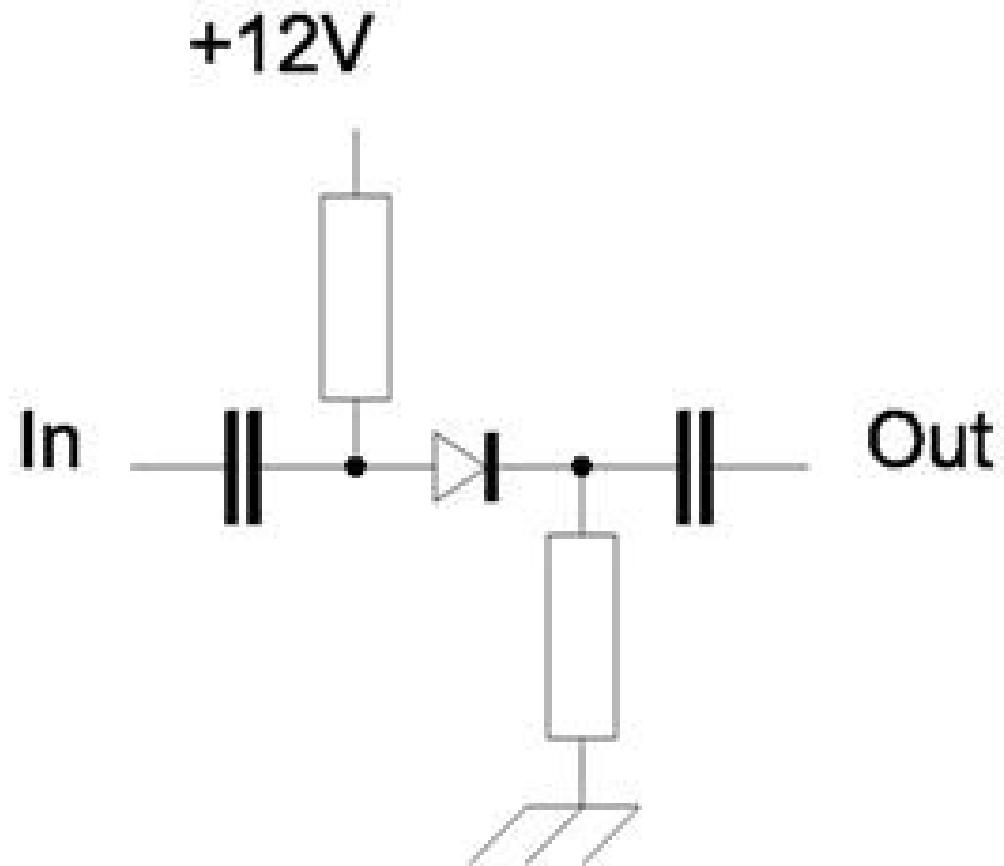


Switching


- ▶ Radio Frequencies

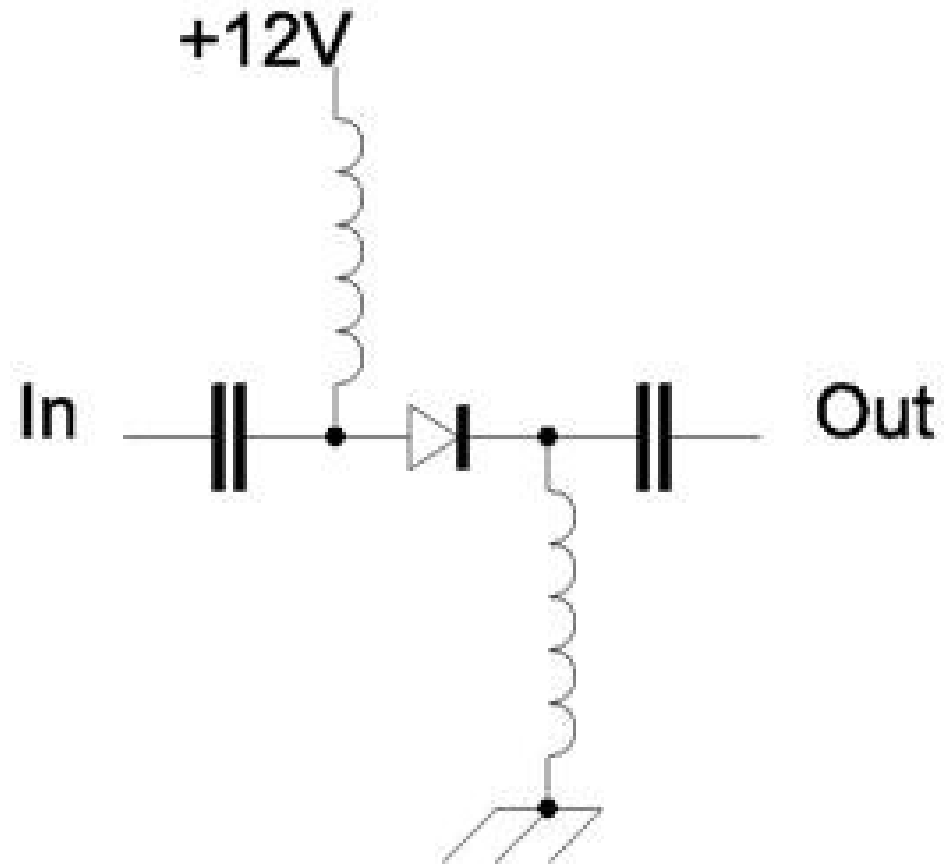

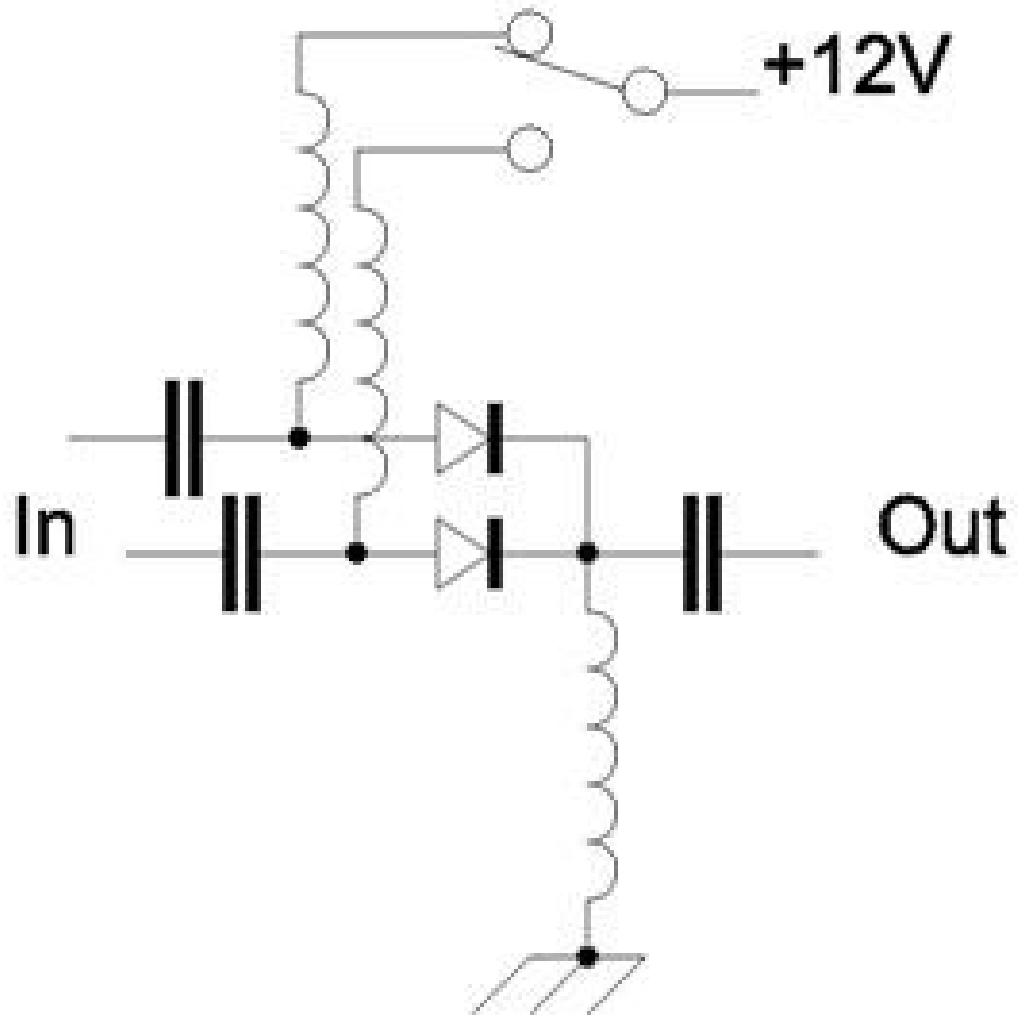


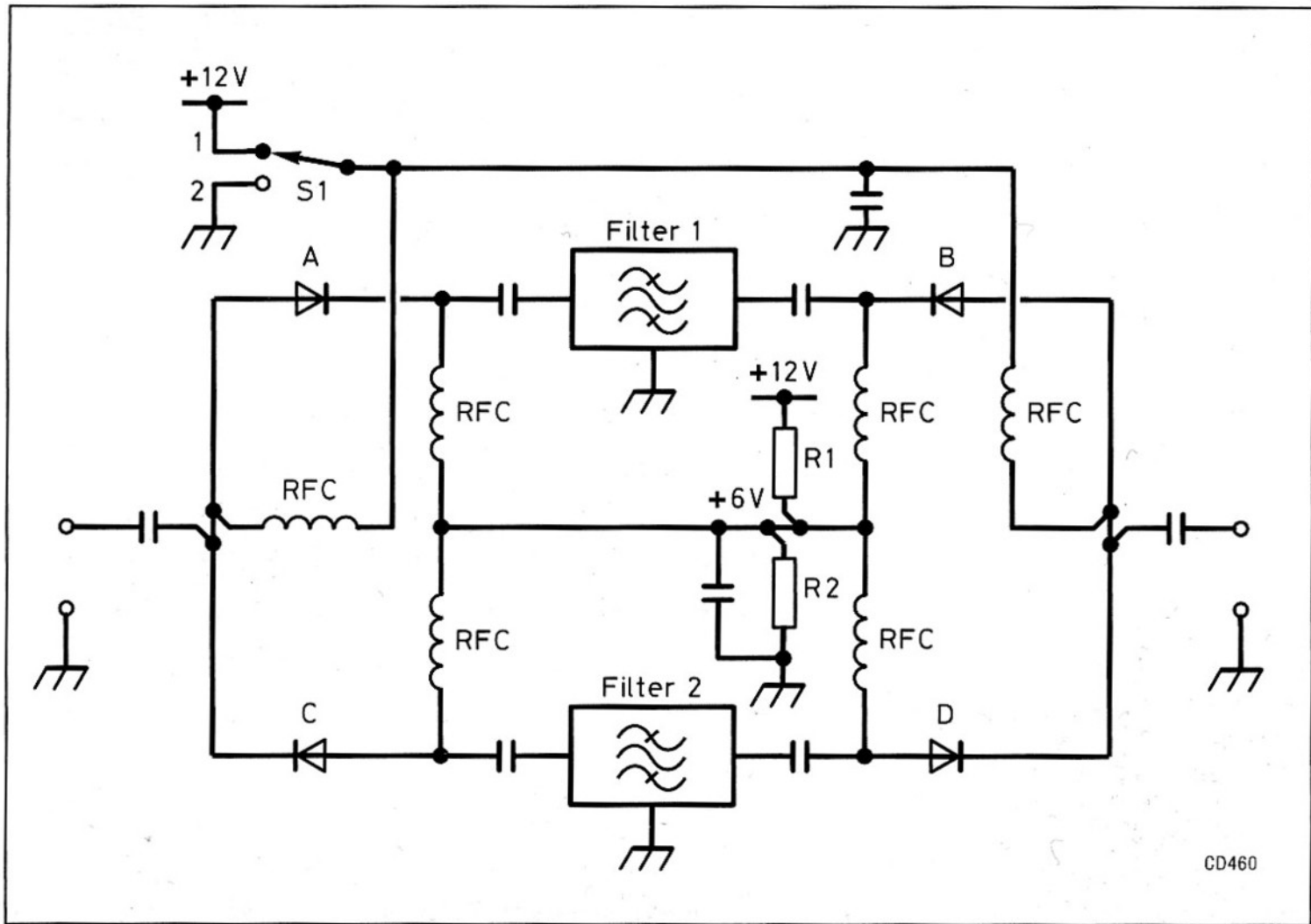

CD460

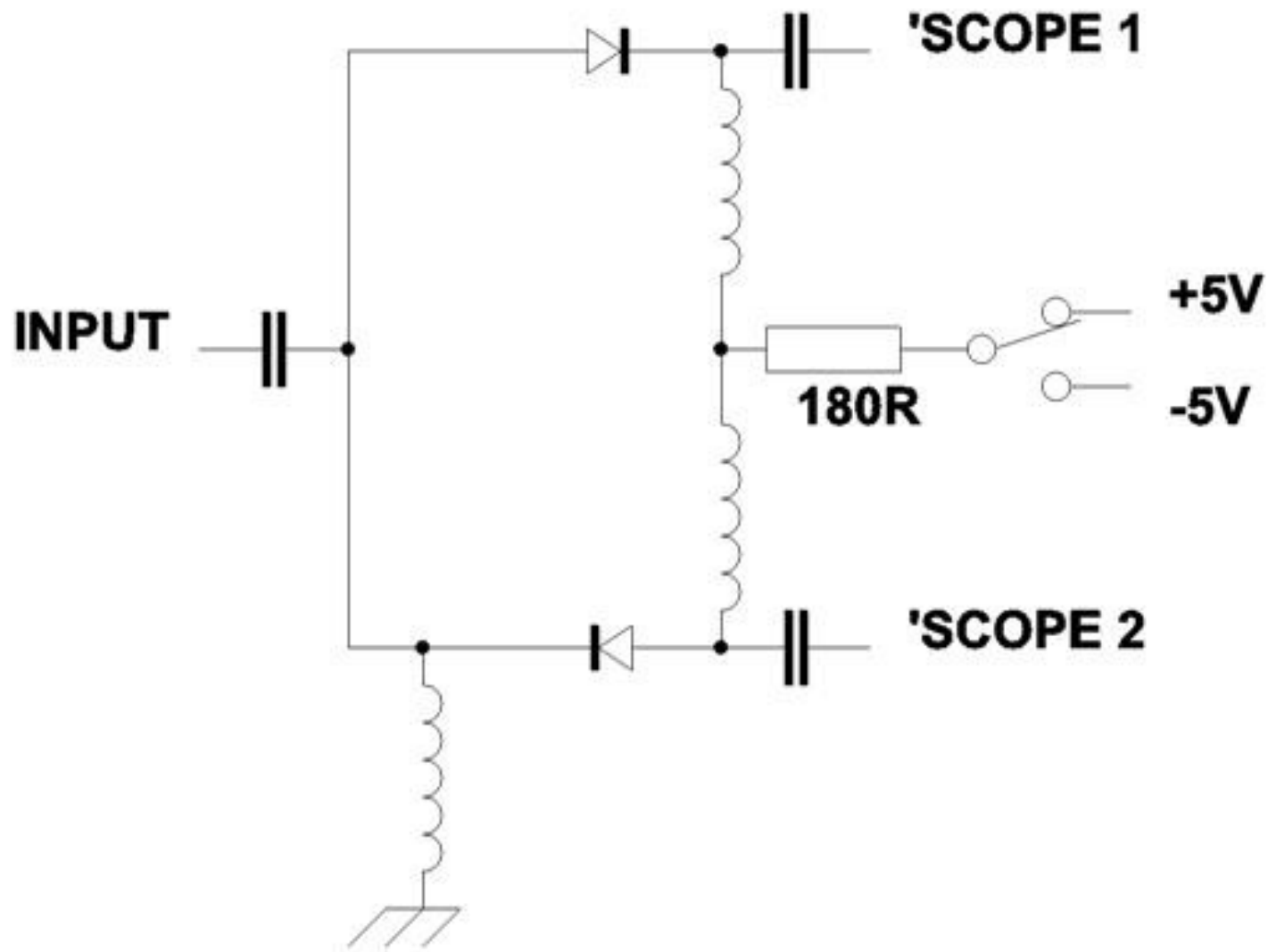


FT817

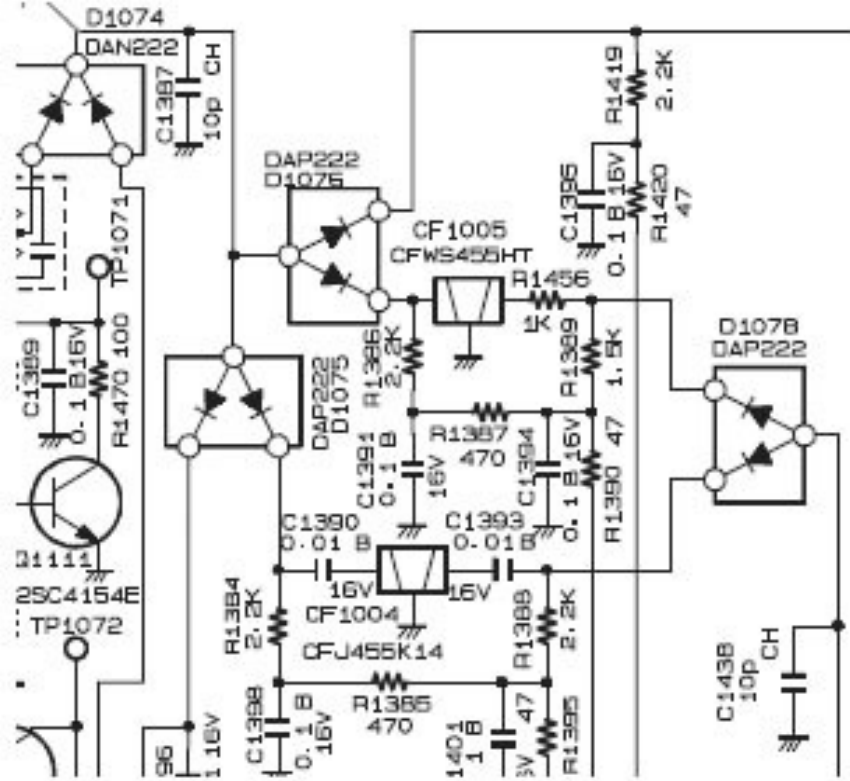



FT980


IF UNIT

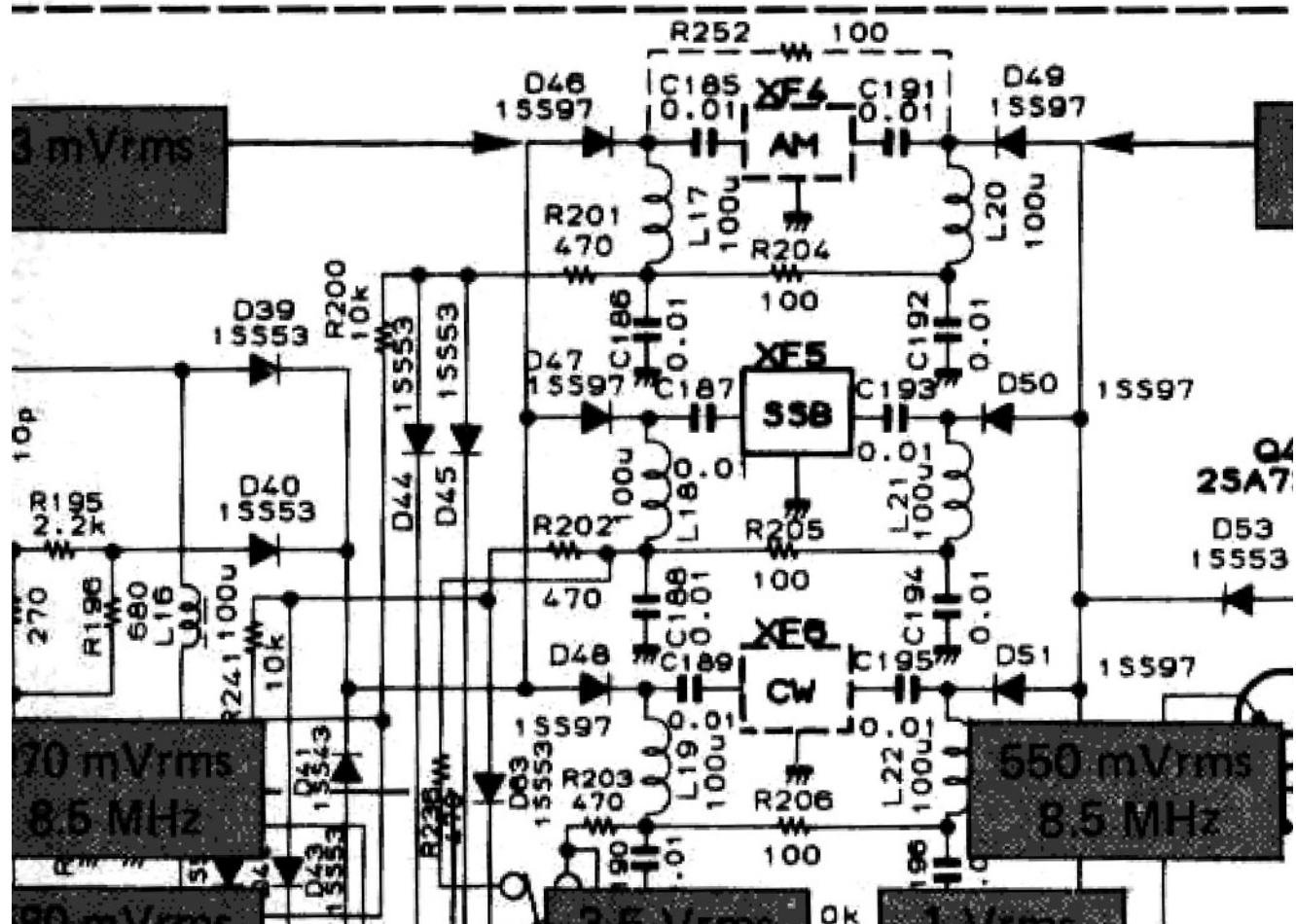



Diode Matrix

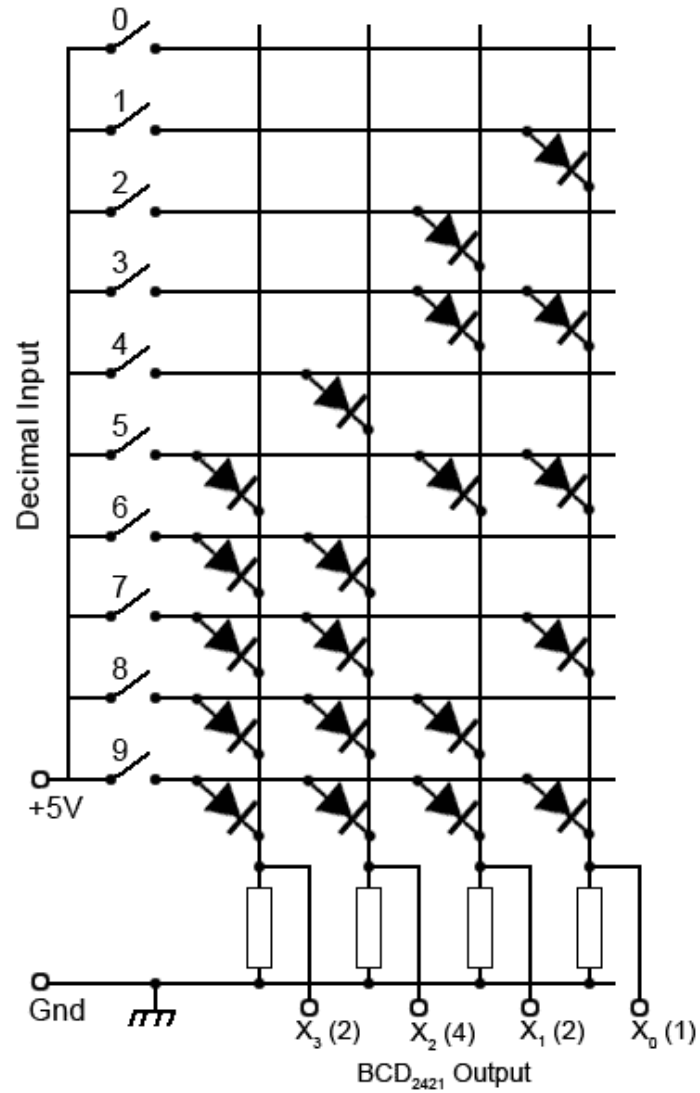

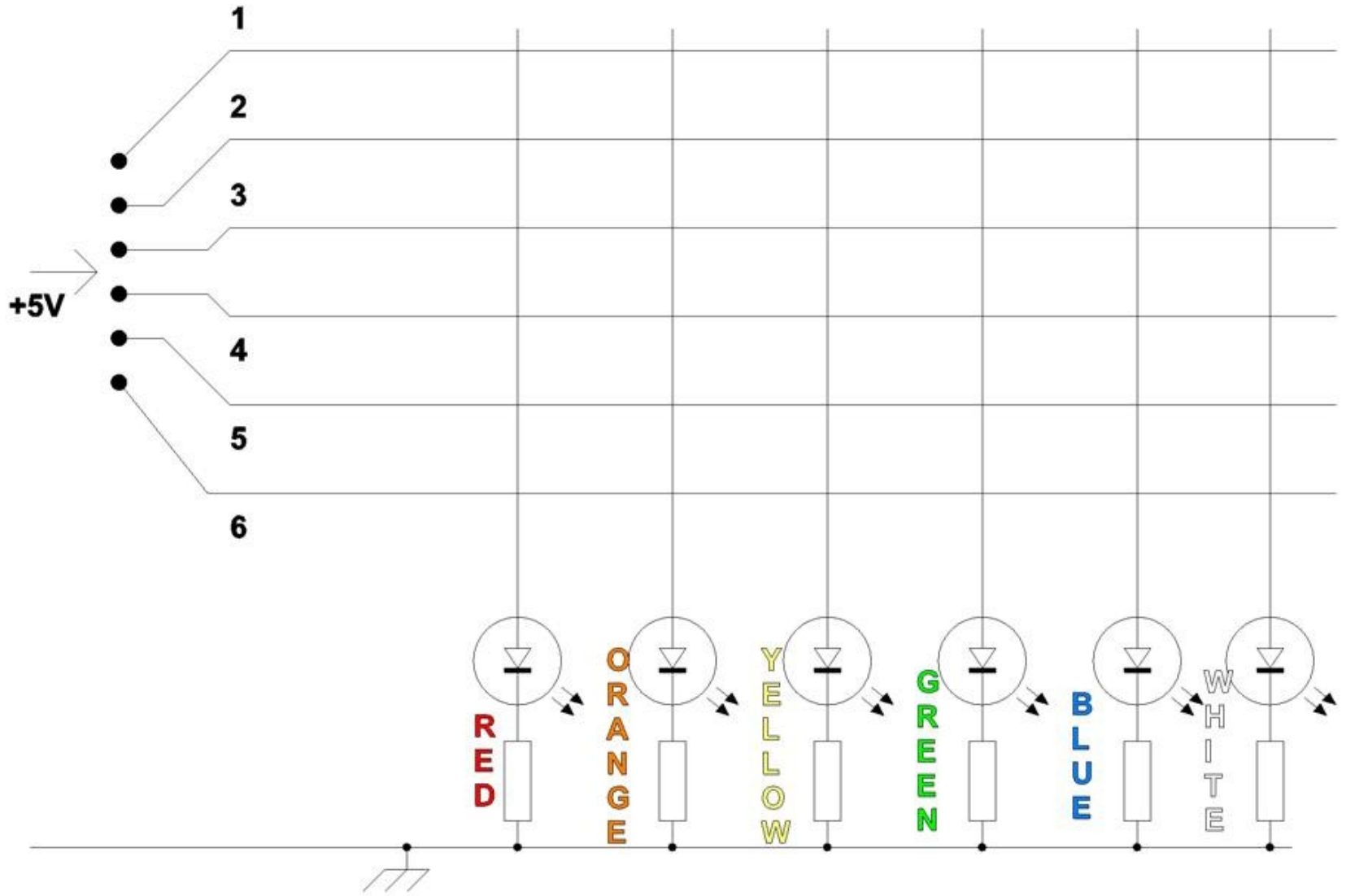

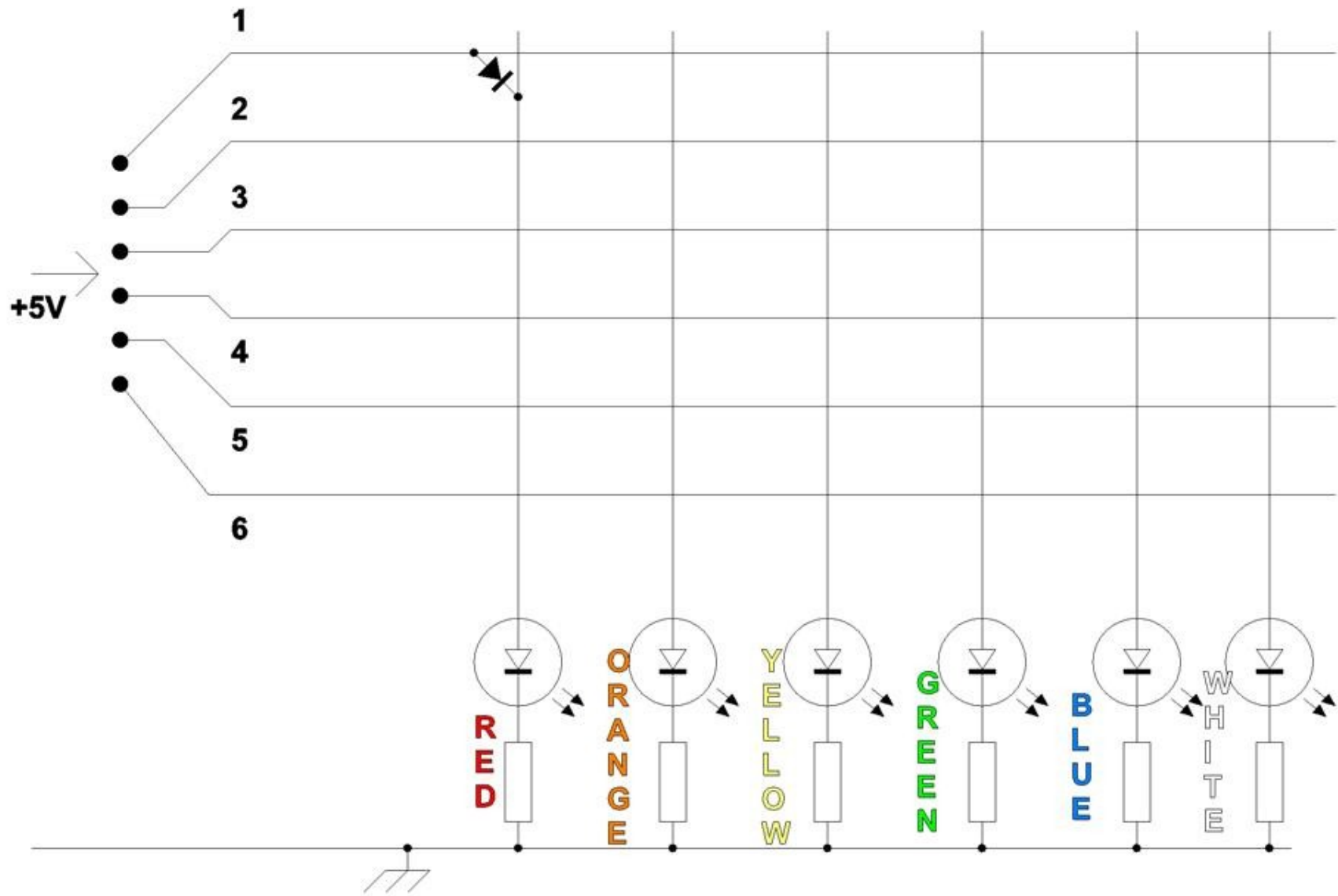


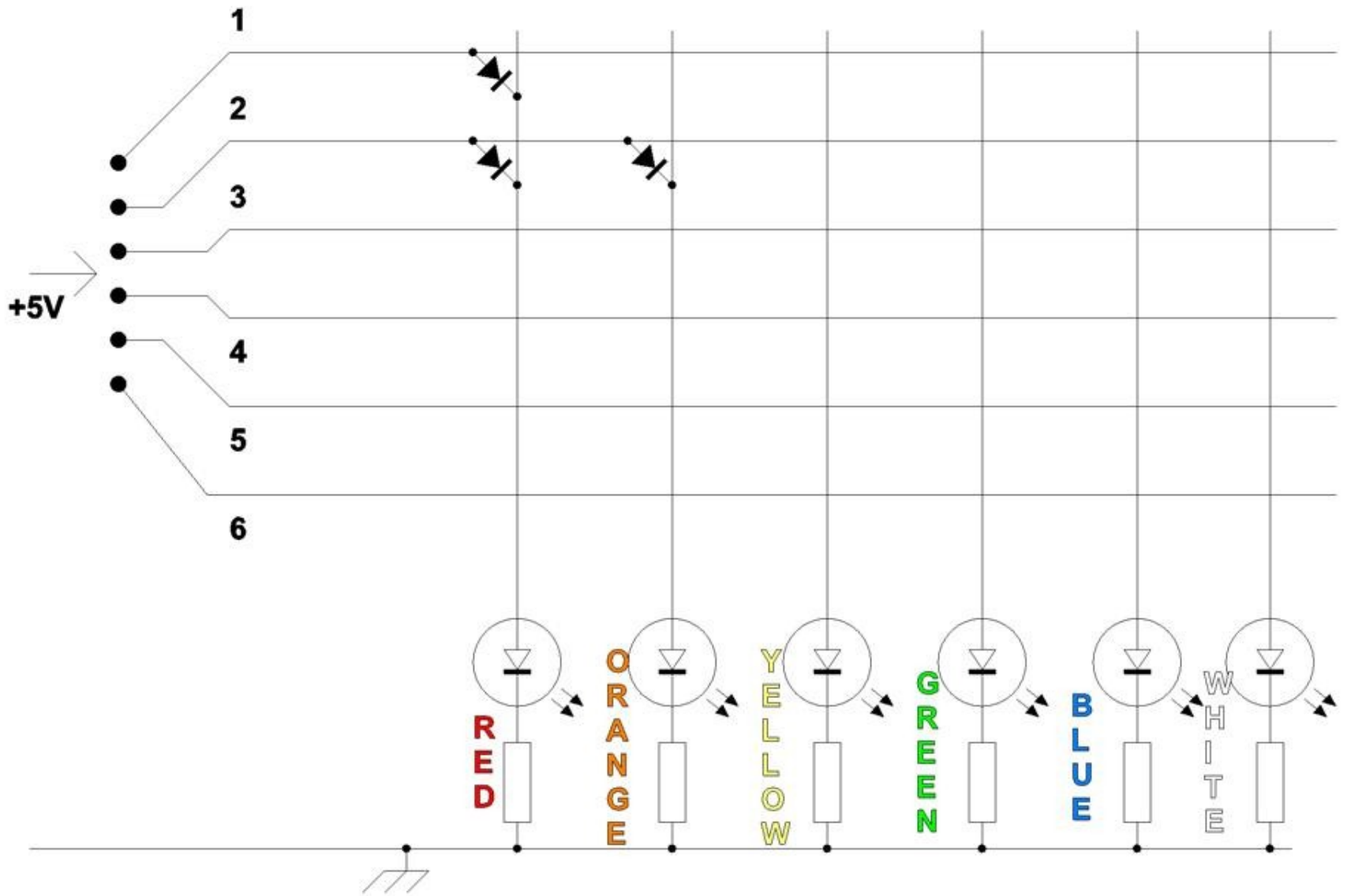


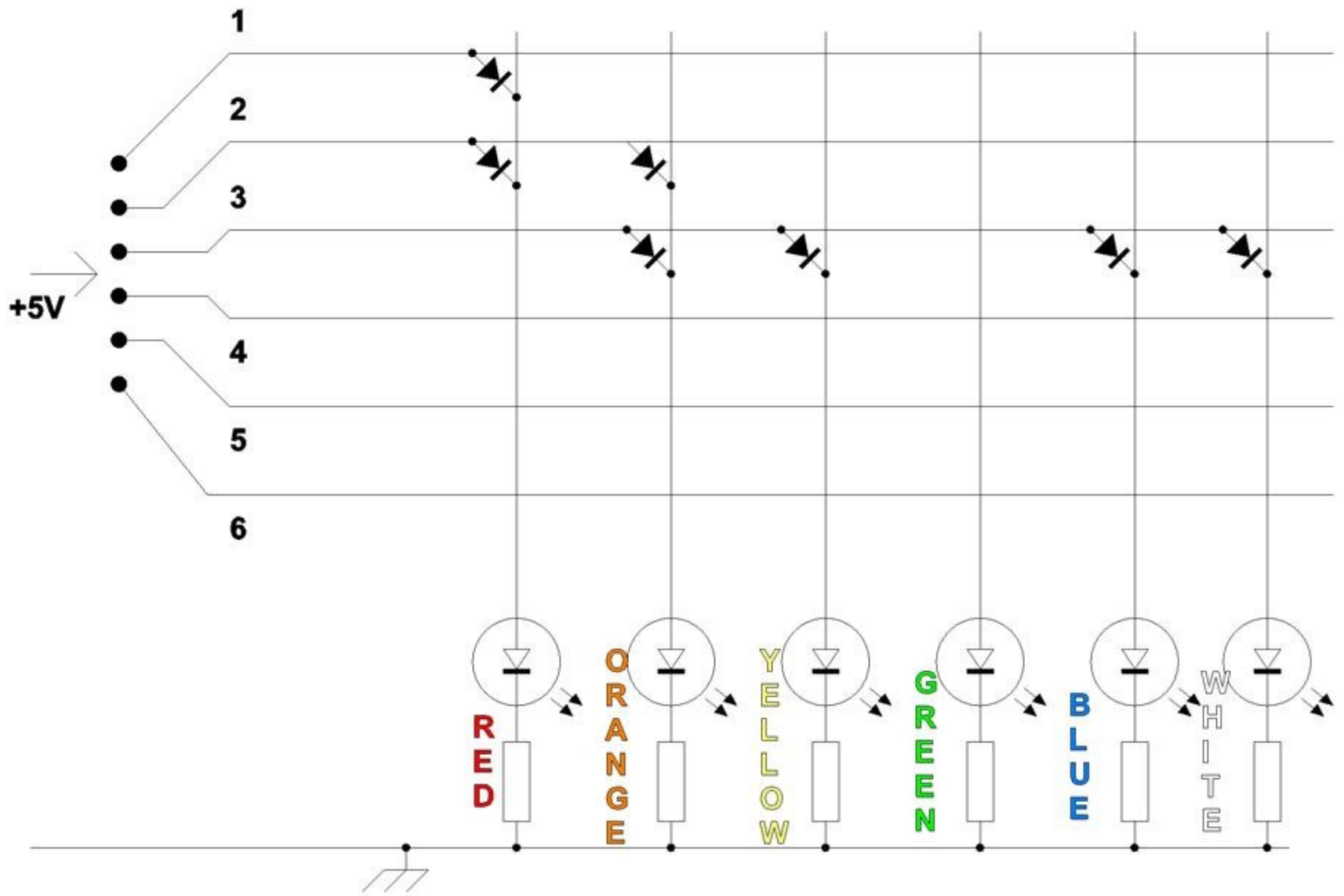

Protection

Signal Source.

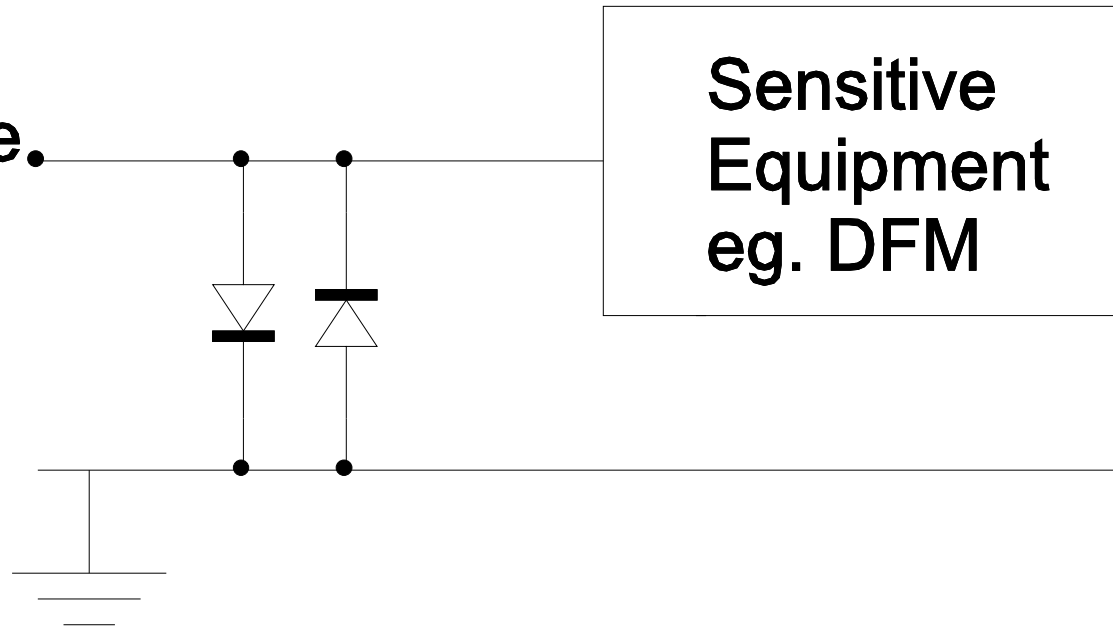

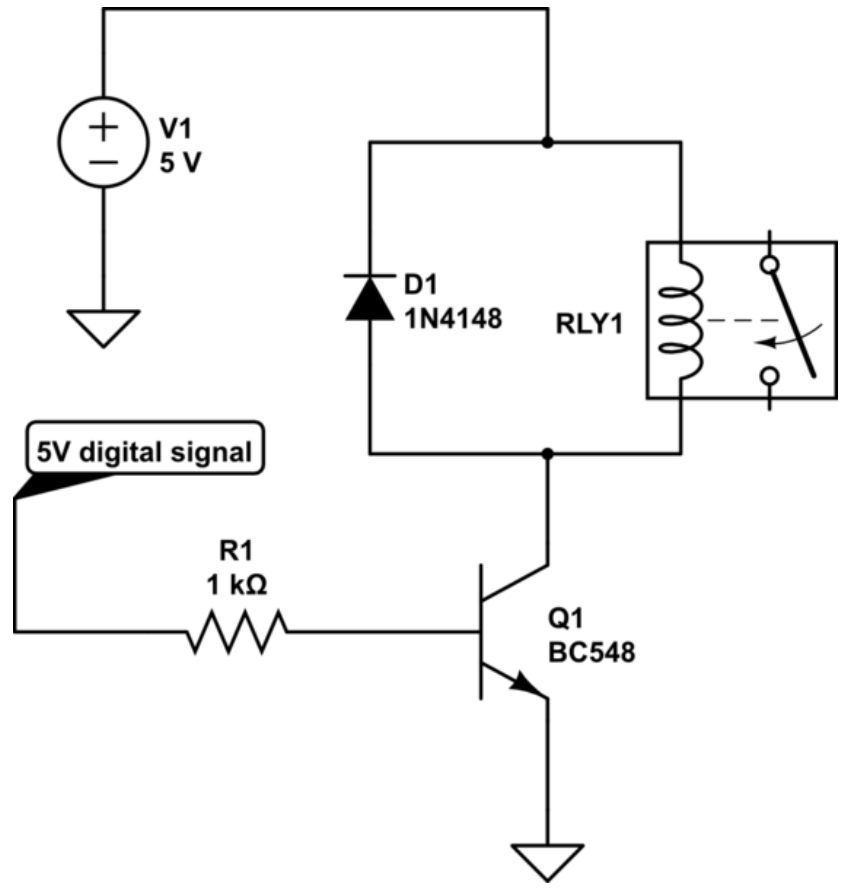


Bias Tee

- ▶ How can we get water and wine down the same pipe at the same time– and separately?

Bias Tee

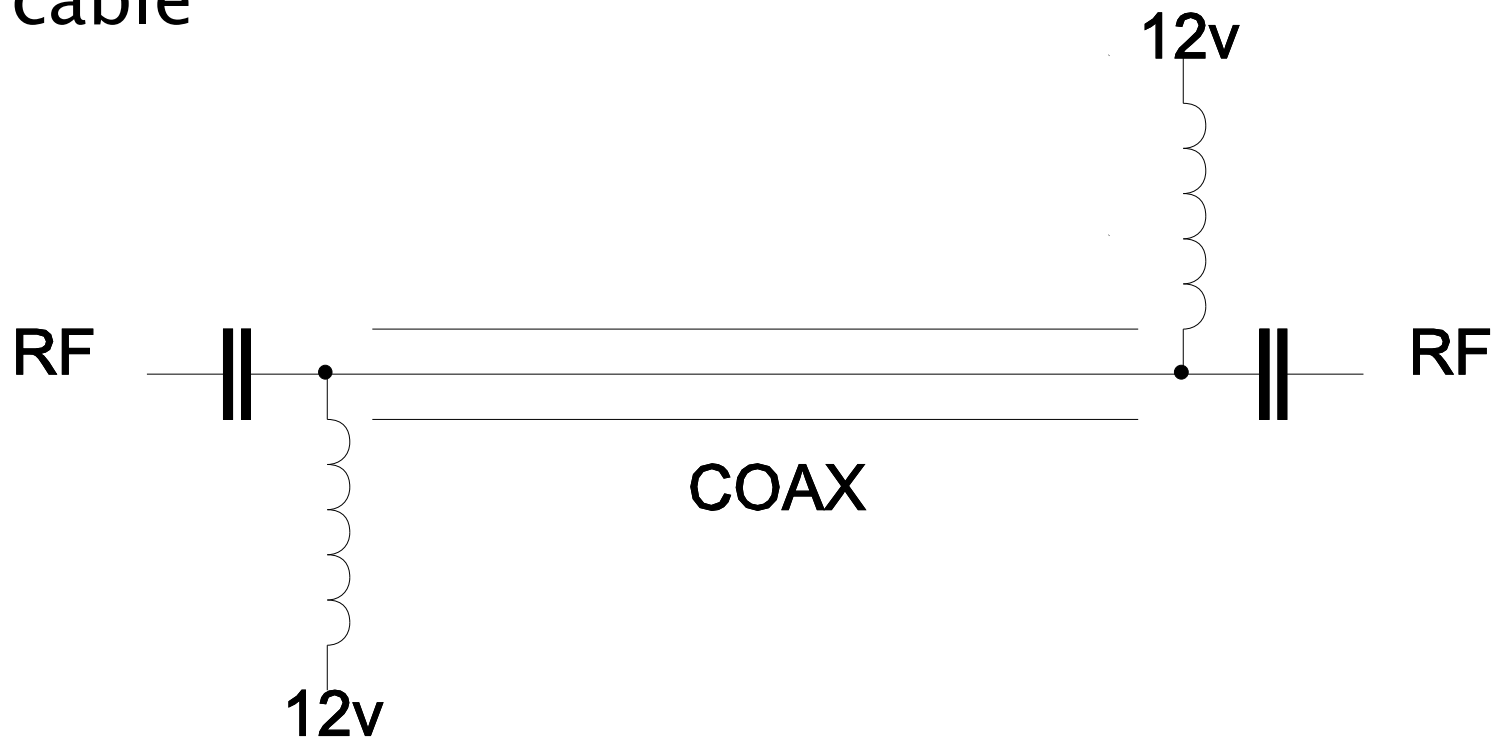- ▶ Enables DC and Signal to pass along a single cable



Bias Tee





That's all Folks!



GX3SBL

Stafford and Districts
Amateur Radio Society